

EHB205E Introduction to Logic Design

Quiz 2

Duration: 45 Minutes


Grading: 1) 40%, 2) 60%

Quiz is in closed-notes and closed-books format


For your answers please use the space provided in the exam sheet

GOOD LUCK!

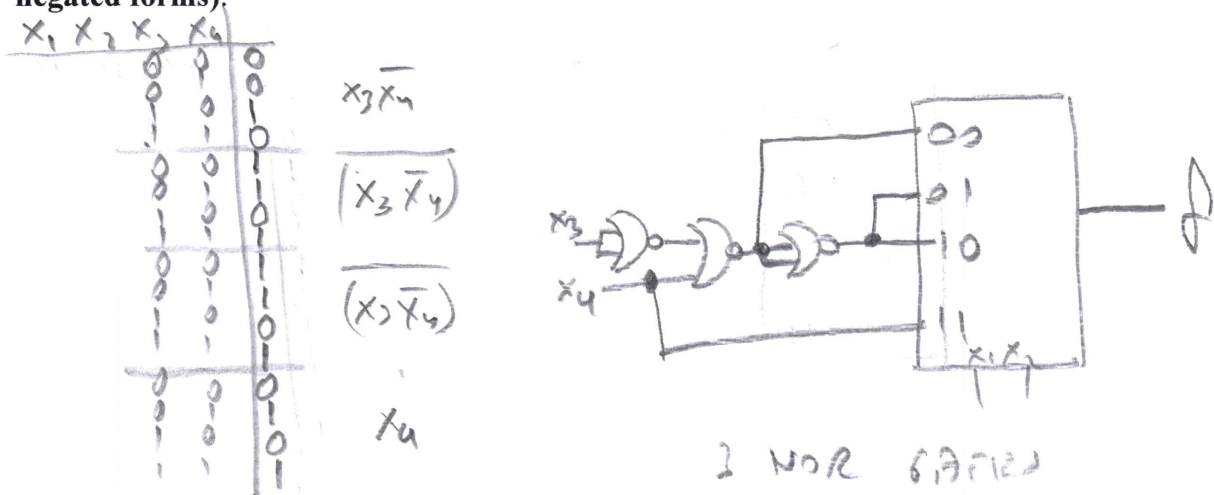1. Implement a 4-variable Boolean function $f(x_1, x_2, x_3, x_4) = \sum(2,4,5,7,8,9,11,13,15)$ using a single 4-to-1 multiplexer and minimal number of two-input NOR gates. Use x_1 and x_2 as select input lines in the multiplexer. Use only variables x_1, x_2, x_3, x_4 as inputs (not their negated forms).



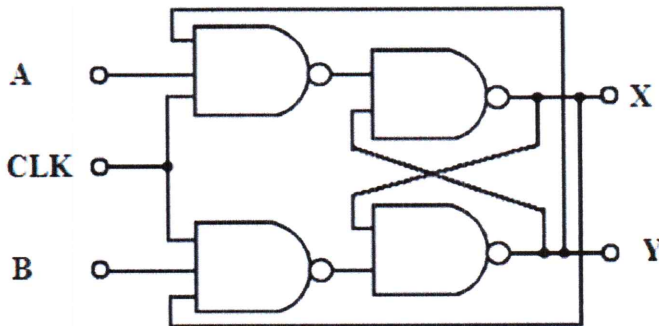2. Consider a sequential circuit shown below. It has three input A, B, and CLK and two outputs X and Y. Obtain its truth table, and Boolean expressions for X and Y.



CLK=0 HOLD CLK=1
 $X = X_{pre}$ $Y = Y_{pre}$

A	B	X	Y
0	0	X_{pre}	Y_{pre}
0	1	0	1
1	0	1	0
1	1	\bar{X}_{pre}	\bar{Y}_{pre}

toggle

$$X = \overline{CLK} X_{pre} + A \bar{B} X_{pre} + CLK AB + CLK A \bar{B} \bar{X}_{pre}$$

$$Y = \overline{CLK} Y_{pre} + \bar{A} B Y_{pre} + CLK \bar{A} B + CLK A \bar{B} \bar{Y}_{pre}$$