

Student Name:

Instructor: Mustafa Altun

Student ID:

Date: 24/12/2021

## EHB205E Introduction to Logic Design MIDTERM II

Duration: 120 Minutes

Grading: 1) 20%, 2) 20%, 3) 25%, 4) 35%

Exam is in closed-notes and closed-books format; calculators are allowed


For your answers please use the space provided in the exam sheet

GOOD LUCK!

- 1) Consider Boolean functions  $f_1(x_1, x_2, x_3) = \sum (0, 1, 3, 5, 6, 7)$  and  $f_2(x_4, x_5, x_6) = \sum (2, 3, 4, 5, 6, 7)$ . Implement  $f = f_1 + f_2$  using **two 3-to-8 decoders** and minimal number of **two-input NOR gates**.

$$f_1 = \prod (2, 4)$$

$$f_2 = \prod (0, 1)$$

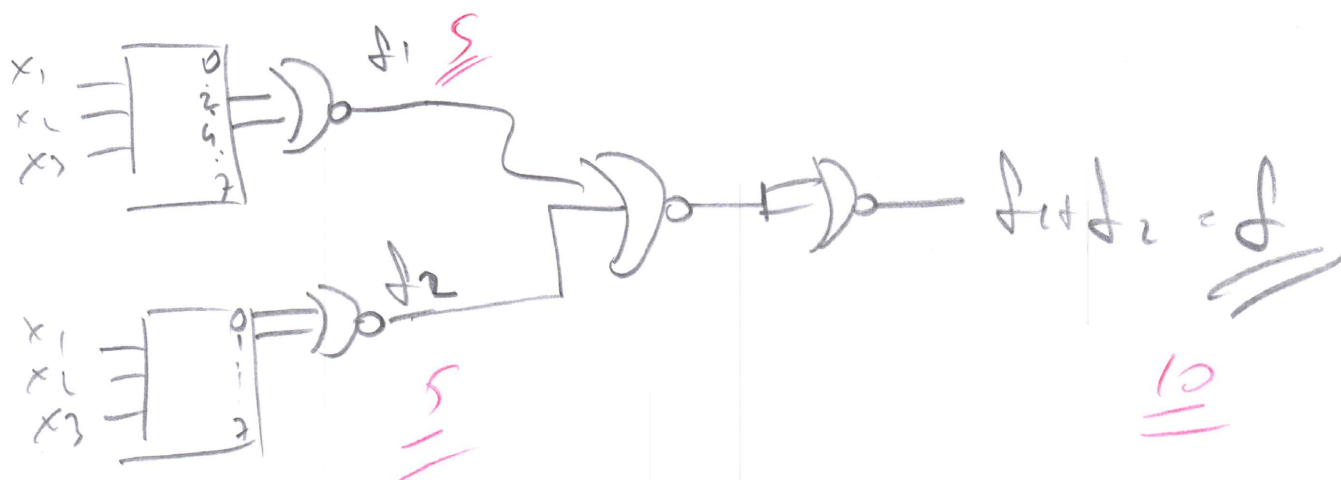

2) Consider a **6-to-1 multiplexer** having inputs  $I_0, I_1, I_2, I_3, I_4, I_5$ ; select input  $S_0, S_1, S_2$ ; and the output OUT.

If  $(S_0, S_1, S_2) = (0, 0, 0)$  then  $OUT = I_0$ ;

If  $(S_0, S_1, S_2) = (0, 0, 1)$  then  $OUT = I_1$ ;


If  $(S_0, S_1, S_2) = (0, 1, 0)$  then  $OUT = I_2$ ;

If  $(S_0, S_1, S_2) = (0, 1, 1)$  then  $OUT = I_3$ ;


If  $(S_0, S_1, S_2) = (1, 0, 0)$  then  $OUT = I_4$ ;

If  $(S_0, S_1, S_2) = (1, 0, 1)$  then  $OUT = I_5$ .

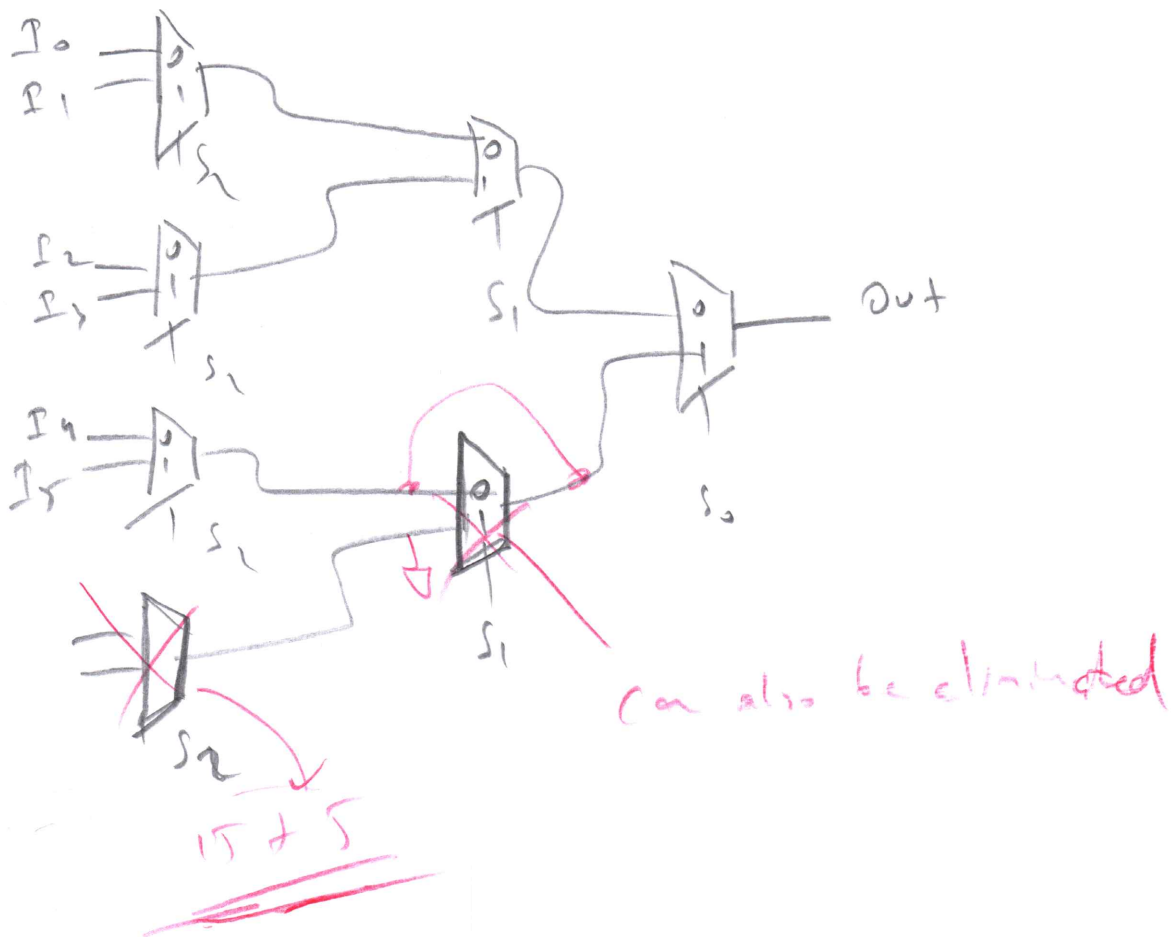Implement this 6-to-1 multiplexer multiplier using **minimal number of 2-to-1 multiplexers**.



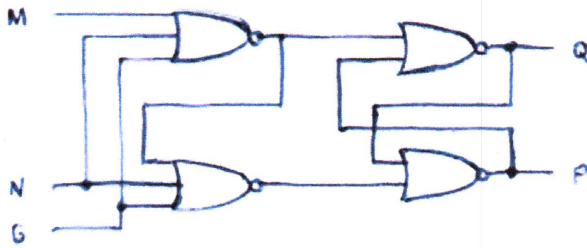3) Consider a sequential circuit shown below.



- a) For which input values of M, N, and G, outputs P and Q hold their previous values?  
b) Obtain a minimal sum-of-products (SOP) expressions for P and Q in terms of M, N, and G as well as the previous values of P and Q.

$$a) \quad N = 1 \quad \text{OR} \quad \underline{G} = 1 \quad \Rightarrow \quad Q = Q_P \quad P = P_P$$

$$b) \quad N = 0 \quad \text{AND} \quad G = 0 \quad \Rightarrow \quad Q = M \quad P = \overline{M}$$

$$Q = Q_P (N + G) + M (\overline{N} \overline{G}) \quad \underline{\underline{10}}$$

$$P = P_P (N + G) + \overline{M} (\overline{N} \overline{G}) \quad \underline{\underline{10}}$$

- 4) Consider a flip-flop consisting of four NAND gates, shown below. Suppose that each of the NAND gates has a delay of **2ns**. Suppose that initial values of  $Q$  and  $Q'$  are 0 and 1, respectively. Sketch the **waveforms at the outputs  $Q$  and  $Q'$**  if the input signals  $A$  and  $CLK$  shown below are applied.

