

Student Name:

Instructor: Mustafa Altun

Student ID:

Date: 03/12/2019

EHB205E Introduction to Logic Design

MIDTERM II

Duration: 120 Minutes

Grading: 1) 20%, 2) 20%, 3) 20%, 4) 40%

Exam is in closed-notes and closed-books format; calculators are allowed


For your answers please use the space provided in the exam sheet

GOOD LUCK!

- 1) Consider a Boolean function $f = (x_1x_2x_3x_4x_5x_6) + (x_1 + x_2 + x_3 + x_4x_5x_6)'$. Use only variables $x_1, x_2, x_3, x_4, x_5, x_6$ as inputs (**not their negated forms**). Implement f using **two 3-to-8 decoders** and **minimal number of two-input NAND gates**.

- 2) Implement a 4-variable Boolean function $f(x_1, x_2, x_3, x_4) = \sum(1,4,6,7,12,14,15)$ using **minimal number of 2-to-1 multiplexers**. Use only variables x_1, x_2, x_3, x_4 as inputs (**not their negated forms**). You can also use 0's and 1's as inputs.

 - 3) Consider a sequential circuit shown below. It has three input A, B, and CLK and two output X and Y. **Obtain its truth table.**



- 4) Consider a flip-flop consisting of one inverter, one XOR gate, and four NAND gates, shown below. Suppose that the inverter has a delay of **1ns**; each of the NAND gates has a delay of **3ns**; the XOR gate has a delay of **5ns**. Sketch the **waveforms at the outputs Q and Q'** if the input signals A and CLK shown below are applied. Suppose that initial values of Q and Q' are 0 and 1, respectively.

