

Student Name:


Student ID:

Date: 15/11/2012

## EHB262E Electronics II

### Quiz 1

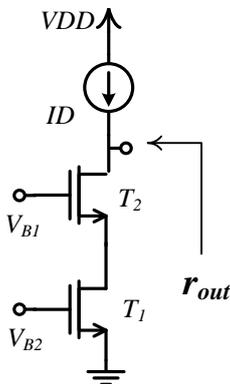- 1) Please circle TRUE if you think that the statement is true; FALSE otherwise.
- a. Voltage amplifiers preferably have high output resistances.  
TRUE / FALSE
  - b. Transresistance amplifiers preferably have low output resistances.  
TRUE / FALSE
  - c. BJTs have threshold values under which they are in cut-off region.  
TRUE / FALSE
  - d. Small signal models are for finding DC operating points.  
TRUE / FALSE
  - e. Gain of an amplifier depends on its load resistance.  
TRUE / FALSE
- 2) Suppose that  $I_D$  is an ideal current source, and both  $V_{B1}$  and  $V_{B2}$  are DC bias voltages. Determine the small signal output resistance  $r_{out}$  in terms of  $g_{m1}$ ,  $g_{m2}$ ,  $r_{o1}$ , and  $r_{o2}$  (not necessarily all of them).



Grading: 1) 50% (10% each), 2) 50%

Duration: 15 minutes