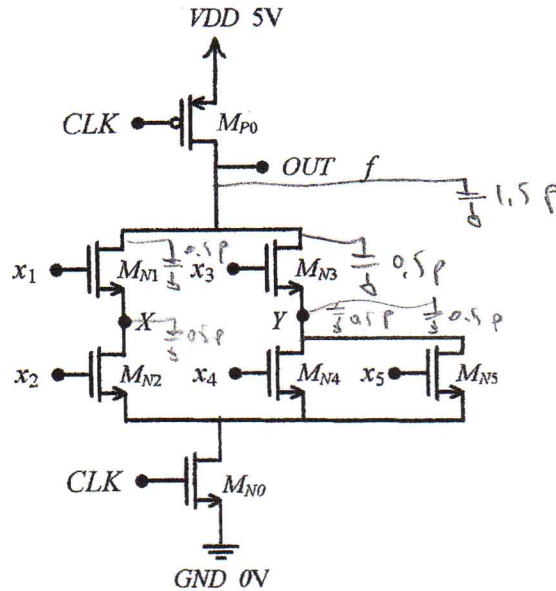


- Suppose that each transistor has an internal grounded gate capacitor  $C_G$  and drain capacitor  $C_D$ :  
 $C_G = c_{ox} W L$ ;  $C_D = (c_{ox} W L)/2$ ;  $c_{ox} = 1 \text{ pF}/\mu\text{m}^2$ .
- Suppose that all NMOS transistors are identical and all PMOS transistors are identical.
- $W_{N0} = W_{N1} = W_{N2} = W_{N3} = W_{N4} = W_{N5} = 1 \mu$ ,  $W_{P0} = 3 \mu$ , and  $V_{TN} = |V_{TP}| = 1 \text{ V}$ .



Dynamic Logic Circuit

- Derive a Boolean expression of  $f$  in terms of the inputs  $x_1$  through  $x_5$  in evaluation phase.
- At the start of the evaluation phase suppose that  $x_1 = 0 \rightarrow 1$ ,  $x_2 = 0$ ,  $x_3 = 0 \rightarrow 1$ ,  $x_4 = 0$ ,  $x_5 = 0$ , and  $V_X = 0 \text{ V}$ ,  $V_Y = 0 \text{ V}$ ,  $V_{OUT} = 5 \text{ V}$ . Considering the charge share problem, find the final voltage value at the output.
- To make the final voltage value at the output as  $4.5 \text{ V}$ , determine the capacitor value of a load to drive.

20 a)  $f = (x_1 x_2 + x_3 (x_4 + x_5))$

20

b)  $C_L = 1.5 \text{ pF} + 0.5 \text{ pF} + 0.5 \text{ pF} = 2.5 \text{ pF}$

$C_X = 0.5 \text{ pF}$        $C_Y = 1 \text{ pF}$

Assume that  $OUT_{final} \geq (V_{DD} - V_T)$ ;  $V_X_{final} = 4 \text{ V}$      $V_Y_{final} = 4 \text{ V}$

50  $\Rightarrow 4 \text{ V} \cdot 0.5 \text{ pF} + 4 \text{ V} \cdot 1 \text{ pF} \leq 2.5 \text{ pF} \cdot 1 \text{ V}$     X assumption is wrong

$\Rightarrow OUT_{final} = V_X_{final} = V_Y_{final} = V_f \leq 4 \text{ V}$

25

$(2.5 \text{ pF}) \cdot (5 - V_f) = 1 \text{ pF} \cdot V_f + 0.5 \text{ pF} \cdot V_f$

$\Rightarrow 12 \text{ pF} = 4 \text{ pF} \cdot V_f \Rightarrow V_f = 3.125 \text{ V}$

25

50 c)  $(5 - 4.5) C_L = 4 \cdot 0.5 \text{ pF} + 4 \cdot 1 \text{ pF} \Rightarrow C_L = 12 \text{ pF}$

Additional cap = 9.5 pF

15