

Student Name:

Instructor: Mustafa Altun

Student ID:

Date: 20/04/2015

# EHB222E Introduction to Electronics MIDTERM II

Duration: 120 Minutes


Grading: 1) 30%, 2) 30%, 3) 40%

Exam is in closed-notes and closed-books format; calculators are allowed

For your answers please use the space provided in the exam sheet

GOOD LUCK!


- 1) Consider an amplifier shown below. Suppose that the value of  $C_c$  is high enough, so it can be considered shorted in small signal analysis. Find the small signal values of  $r_{in}$ ,  $r_{out}$ , and  $v_{out}/v_{in}$ .  
PNP Transistor Parameters:  $|V_{BE}| = 0.7$ ,  $\beta = 100$ ,  $|V_A| = 10V$ ,  $V_T = 25$  mV.

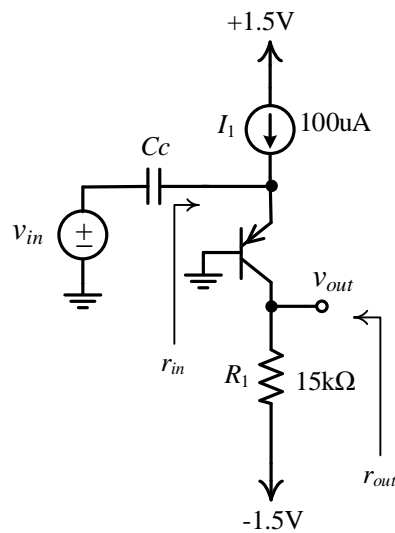

Common Base Amplifier.

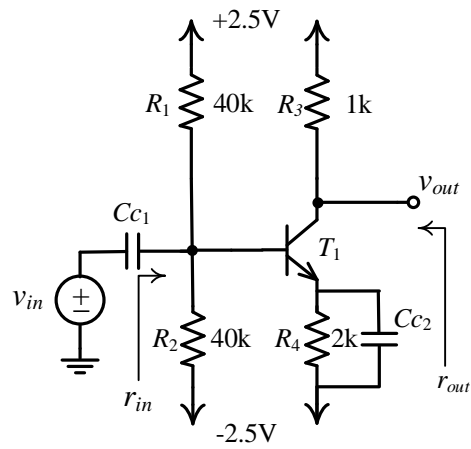
- 2) Consider an amplifier shown below. Suppose that the value of the coupling capacitors  $C_{c1}$  and  $C_{c2}$  are high enough, so they can be considered shorted in small signal analysis. Find the small signal values of  $r_{in}$ ,  $r_{out}$ , and  $v_{out}/v_{in}$ .

*NPN Transistor Parameters:  $V_{BE} = 0.7$ ,  $\beta = 40$ ,  $V_A = \infty$ ,  $V_T = 25$  mV.*



*Common Emitter Amplifier*

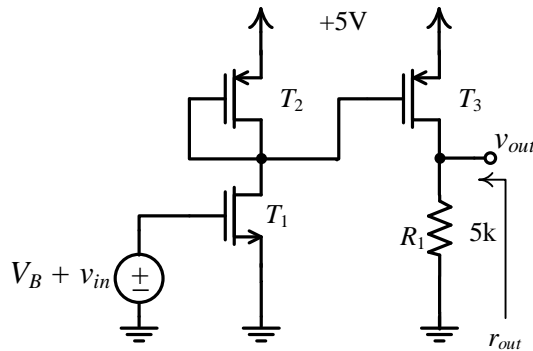- 3) Consider a two-stage amplifier shown below. Suppose that  $V_B = 2\text{V}$ . All PMOS transistors are identical. Determine the small signal output resistance  $r_{out}$  and the gain  $v_{out}/v_{in}$ .



Two-Stage Amplifier

Transistor parameters:  $k_p' = \mu_p c_{ox} = 50 \mu\text{A}/\text{V}^2$ ,  $k_n' = \mu_n c_{ox} = 100 \mu\text{A}/\text{V}^2$ ,  $V_{An} = |V_{Ap}| = 25\text{V}$ ,  $V_{T,n} = 1\text{V}$ ,  $V_{T,p} = -1\text{V}$ ,  $W_{P2} = 32\mu$ ,  $L_{P2} = 1\mu$ ,  $W_{P3} = 80\mu$ ,  $L_{P3} = 1\mu$ ,  $W_{n1} = 4\mu$ ,  $L_{n1} = 1\mu$ .

- In DC analysis, neglect the Early effect and use the following equation:

$$I_D = \frac{1}{2} k'_{p,n} \frac{W}{L} (V_{GS} - V_{T,p,n})^2.$$

- In small analysis you should consider the Early effect.
- To find the gain ( $v_{out}/v_{in}$ ) of the amplifier, you need to find the gain of each stage.