

# QUIZ 1 SOLUTIONS

1.) a)  $(1001, 100)_2$   
 $2^3 \ 2^2 \ 2^1 \ 2^0 \ 2^{-1} \ 2^{-2} \ 2^{-3} \ 2^{-4}$

$$1+8, \frac{1}{2} + \frac{1}{16} = (9,5625)_{10}$$

b)  $(72, 6)_8 = (58,75)_{10}$   
 $8^1 \ 8^0 \ 8^{-1}$

$58 / 2 = 29$	+	0	111010
$29 / 2 = 14$	+	1	
$14 / 2 = 7$	+	0	
$7 / 2 = 3$	+	1	
$3 / 2 = 1$	+	1	
$1 / 2 = 0$	+	1	

$0,75 \times 2 =$	1,5
$0,5 \times 2 =$	1,0

$\Rightarrow (111010, 11)_2$

## 2.) Applying De Morgan Law

$$a) f_1 = (x_1 + \bar{x}_2 + \bar{x}_3)(\bar{x}_1 + \bar{x}_4)$$

$$= x_1 \bar{x}_1 + (x_1 \bar{x}_4 + \bar{x}_2 \bar{x}_1 + \bar{x}_2 \bar{x}_4 + \bar{x}_3 \bar{x}_1 + \bar{x}_3 \bar{x}_4)$$

$$0 + x_1 \bar{x}_4 + \bar{x}_1 \bar{x}_2 + (x_1 + \bar{x}_1) \bar{x}_2 \bar{x}_4 + \bar{x}_1 \bar{x}_3 + \bar{x}_3 \bar{x}_4$$

$$= x_1 \bar{x}_4 + \bar{x}_1 \bar{x}_2 + x_1 \bar{x}_2 \bar{x}_4 + \bar{x}_1 \bar{x}_2 \bar{x}_4 + \bar{x}_1 \bar{x}_3 + \bar{x}_3 \bar{x}_4$$

$$= x_1 \bar{x}_4 + \bar{x}_1 \bar{x}_2 + \bar{x}_1 \bar{x}_3 + \bar{x}_3 \bar{x}_4$$

$$= \bar{x}_1 \bar{x}_2 + (x_1 \bar{x}_4 + \bar{x}_1 \bar{x}_3 + \bar{x}_3 \bar{x}_4) \quad \text{similarly}$$



$$= \bar{x}_1 \bar{x}_2 + x_1 \bar{x}_4 + \bar{x}_1 \bar{x}_3 \quad \text{literal count} = 6$$

$$b) f_2 = (\bar{x}_1 + \bar{x}_2 + x_3)(\bar{x}_1 + x_2 + \bar{x}_3)(x_1 + \bar{x}_2 + \bar{x}_3)(x_1 + x_2 + x_3)$$

$$= x_1 x_2 x_3 + x_1 \bar{x}_2 \bar{x}_3 + \bar{x}_1 x_2 \bar{x}_3 + \bar{x}_1 \bar{x}_2 x_3$$

$$\text{literal count} = 12$$

3.)  
a)

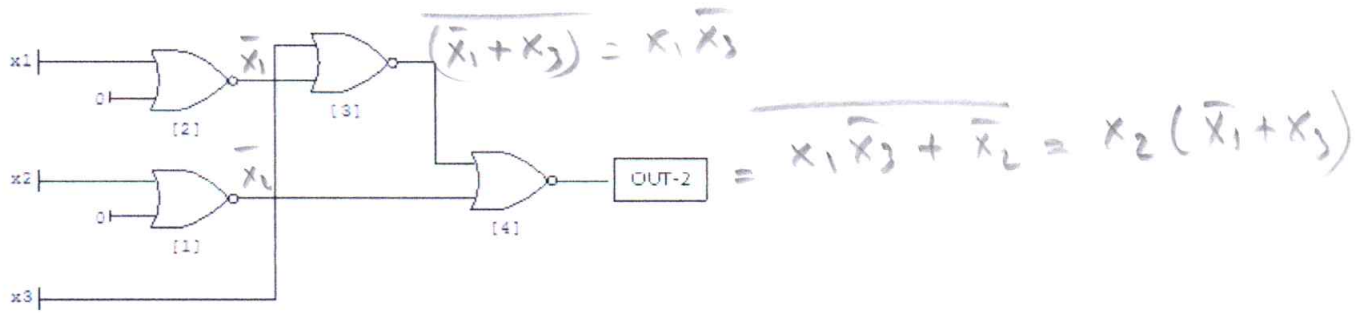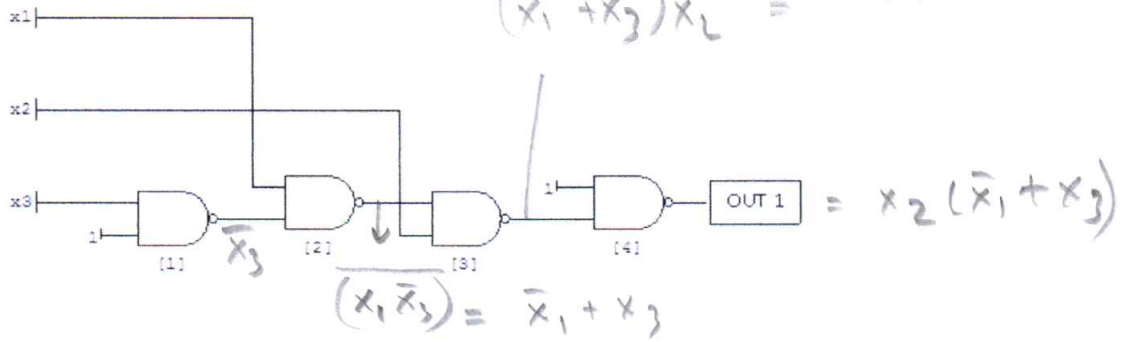


b.)  $\text{OUT 1} = \text{OUT 2} \Rightarrow \text{OUT 1} \oplus \text{OUT 2} = 0$


4.)

$$\begin{aligned}
 a) f_1 &= \overline{(x_1 x_2)} \cdot \overline{(x_2 x_3)} \cdot \overline{(x_3 x_4)} \\
 &= \overline{(x_1 x_2)} \cdot \overline{(x_2 x_3)} \cdot \overline{(x_3 x_4)}
 \end{aligned}$$

7 NAND Gates

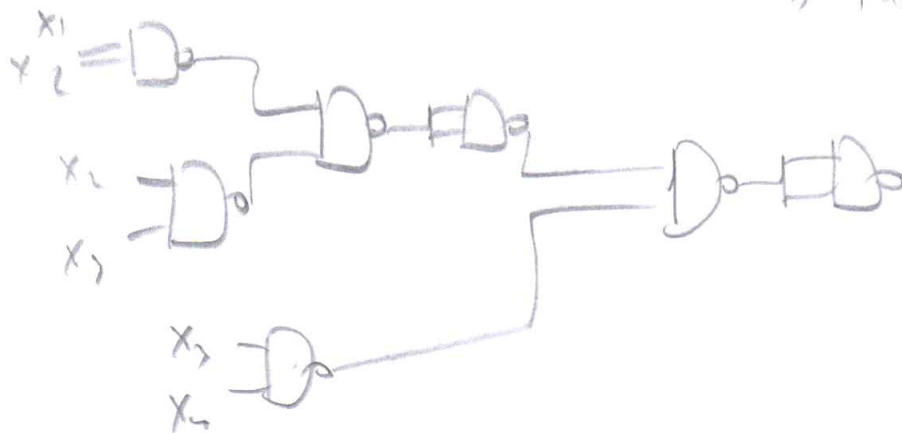
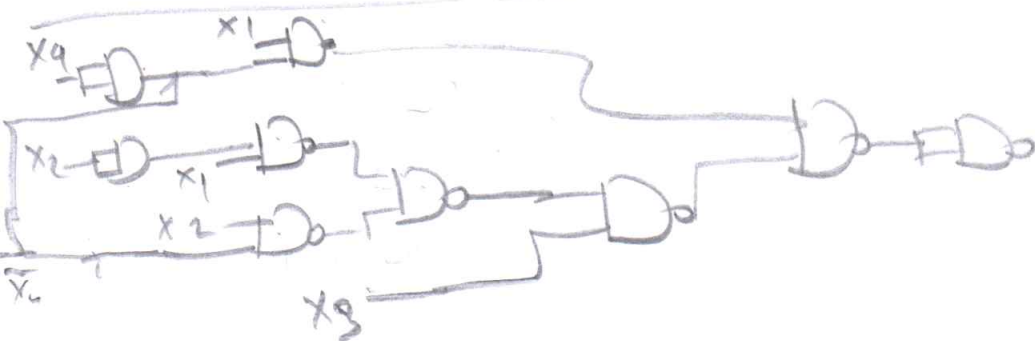
$$\begin{aligned}
 b) f_2 &= x_1 \bar{x}_4 + x_3 (x_1 \bar{x}_2 + x_2 \bar{x}_4) \\
 &= \overline{x_1 \bar{x}_4} \cdot \overline{x_3 (x_1 \bar{x}_2 + x_2 \bar{x}_4)} \\
 &= \overline{(x_1 \bar{x}_4)} \cdot \overline{x_3 (x_1 \bar{x}_2 + x_2 \bar{x}_4)} \\
 &= \overline{x_1 \bar{x}_4} \cdot x_3 \overline{x_1 \bar{x}_2 + x_2 \bar{x}_4}
 \end{aligned}$$



9 NAND gates