

EHB 322-E - HW-2

a) Operation Regions

$$PMOS: |V_{GS} - V_T| = |(0-5) - (-0,95)| = 4,05V \rightarrow V_{satp}$$

$$|V_{DS}| = |5 - 0,2| = 4,8V$$

$$\text{since } |V_{GS} - V_T| \leq |V_{DS}| \rightarrow \text{Saturation}$$

$$4,05 \leq 4,8$$

$$NMOS: |V_{GS} - V_T| = |(5-0) - (0,7)| = 4,3 \rightarrow V_{satn}$$

$$|V_{DS}| = |0,2 - 0| = 0,2$$

$$\text{since } |V_{GS} - V_T| > |V_{DS}| \rightarrow \text{Linear}$$

$$4,3 > 0,2$$

By using current equations, we can find desired W_n value.

$$I_n = I_p$$

$$\frac{\beta_n}{2} [2(V_{GSn} - V_{Tn})V_{DSn} - V_{DSn}^2] = \frac{\beta_p}{2} [V_{GSp} - V_{Tp}]^2$$

$$k_n' \cdot \frac{W_n}{L_n} \cdot [2(4,3)0,2 - (0,2)^2] = k_p' \cdot \frac{W_p}{L_p} [-4,05]^2$$

$$156 \cdot 10^{-6} \cdot W_n (1,68) = 48 \cdot 10^{-6} \cdot 3,2 \cdot 10^{-6} (16,4025)$$

$$W_n = \frac{16,4025 \cdot 48 \cdot 10^{-6} \cdot 3,2 \cdot 10^{-6}}{156 \cdot 10^{-6} \cdot 1,68}$$

$$W_n = 9,62 \cdot 10^{-6} \text{ m} \rightarrow \boxed{9,62 \mu\text{m}}$$

$$b) V_{in} = V_{out} = V_M$$

Operation Regions

$$\text{PMOS: } |V_{GS} - V_{TP}| = 4,05 \text{ V}$$

$$|V_{DS}| = |5 - V_{out}| = |5 - V_M|$$

$$\rightarrow 4,05 \geq |5 - V_M|$$

Linear

$$\text{NMOS: } |V_{GS} - V_{TN}| = |V_M - 0,7|$$

$$|V_{DS}| = |V_M|$$

$$\rightarrow V_M - 0,7 < V_M$$

Saturation

$$\frac{\beta_n}{2} (V_{GS} - V_{TN})^2 = \frac{\beta_p}{2} [2(V_{GSP} - V_{TP})V_{DS} - V_{DS}^2]$$

$$\frac{156 \cdot 10^{-6} \cdot 9,62 \cdot 10^{-6}}{48 \cdot 10^{-6} \cdot 3,2 \cdot 10^{-6}} (V_M - 0,7)^2 = 2 \cdot (-4,05)(V_M - 5) - (V_M - 5)^2$$

$$9,76 \cdot (V_M^2 - 1,4V_M + 0,49) = 40,5 - 8,1V_M - 25 + 10V_M - V_M^2$$

$$10,76V_M^2 - 15,564V_M - 10,716 = 0$$

$$\text{Root 1} \rightarrow 1,955$$

$$\rightarrow \boxed{V_M = 1,955 \text{ V}}$$

$$\text{Root 2} \rightarrow -0,509$$

c) $V_{in} = 0 \rightarrow$ NMOS is off, no current flowing

$$P_S = 0$$

(we could use I_p or $I_n \rightarrow I_p = I_n$)

$$V_{in} = 5 \rightarrow P_S = V \cdot I = 5 \cdot \left[\frac{\beta_P}{2} (V_{GS} - V_T)^2 \right]$$


\rightarrow PMOS in saturation mode bcs of the 0 V input

$$5 \cdot \left[\frac{48 \cdot 10^{-6} \cdot 3,2 \cdot 10^{-6}}{2 \cdot 0,6 \cdot 10^{-6}} \left((0-5) - (-0,85) \right)^2 \right]$$

$$= 5 \cdot 128 \cdot 10^{-6} \cdot 16,4$$

$$= 10497 \cdot 10^{-6} \text{ W} = \boxed{10,49 \text{ mW}}$$

d)

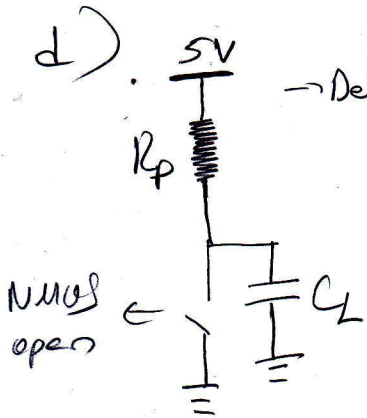

\rightarrow Delay Model

$$t_{PLH} = 0,69 \cdot R_p \cdot C_L$$

$$C_L = 10 \cdot 10^{-12} \text{ F}$$

$$R_p = \frac{1}{2K_p} \cdot \frac{1}{(V_{DD} - |V_{TP}|)} \cdot \left[\frac{2|V_{TP}|}{(V_{DD} - |V_{TP}|)} + \ln \frac{3V_{DD} - 4|V_{TP}|}{V_{DD}} \right]$$

$$K_p = \frac{1}{2} \mu_p \cdot C_{ox} \cdot \frac{W_p}{L_p}$$

$$R_p = \frac{0,6 \cdot 10^{-6}}{48 \cdot 10^{-6} \cdot 3,2 \cdot 10^{-6}} \cdot \frac{1}{4,05} \cdot \left[0,46 + \ln 2,24 \right]$$

$\underbrace{\hspace{10em}}_{964}$
 $\underbrace{\hspace{10em}}_{1,26}$

$$R_p = 1215,2 \Omega$$

$$t_{PLH} = 0,69 \cdot R_p \cdot C_L = 0,69 \cdot 10 \cdot 10^{-12} \cdot 1215,2 = 8384 \cdot 10^{-12}$$

$$\boxed{= 8,3 \text{ ns}}$$