

EHB262E Electronics II, Fall 2012 MIDTERM

Duration: 75 Minutes

Grading: 1) 20% (4% each), 2) 40%, 3) 40% (20%+20%)

Exam is in closed-notes and closed-books format


For your answers please use the space provided in the exam sheet

GOOD LUCK!

- 1) Please circle TRUE if you think that the statement is true; FALSE otherwise.
- a.* While obtaining the small signal gain of an amplifier, all dependent voltage sources should be shorted.
TRUE / FALSE
 - b.* If a voltage amplifier has a 1 Volt DC input and a 3 Volt DC output values then the small signal gain of the amplifier is 3 (3V/1V).
TRUE / FALSE
 - c.* In analog circuits, MOS transistors are preferably operating in triode (linear) region.
TRUE / FALSE
 - d.* Consider two voltage amplifiers with small signal gains of A and B and infinite small signal input resistances. Cascading them results in an amplifier with a small signal gain of $A \times B$.
TRUE / FALSE
 - e.* Consider a current amplifier with a small signal gain of 100 and a small signal output resistance of $3\text{k}\Omega$. If this amplifier drives a load resistance of $1\text{k}\Omega$ then the gain of the amplifier reduces to 75.
TRUE / FALSE

- 2) You are asked to design an amplifier satisfying the following specifications: $r_{in} \geq 200 \text{ k}\Omega$ and $|v_{out}/v_{in}| \geq 10$. Use the amplifier shown below and determine the minimum values of R_E and R_C to meet the specifications where $V_B = 0.95 \text{ V}$.

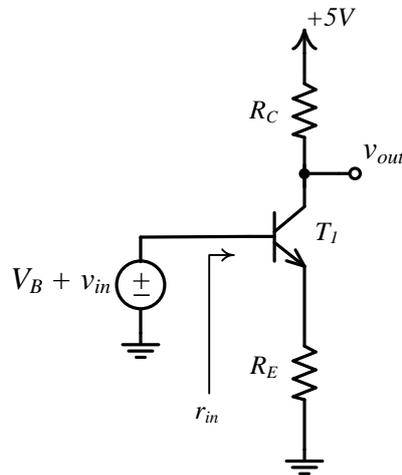Transistor parameters: $V_{BE} = 0.7$, $\beta = 100$, $V_A = 100 \text{ V}$, $V_T = 25 \text{ mV}$.




Common Emitter Amplifier with an Emitter Resistance

- 3) Suppose that $V_B = 1.5V$ and all NMOS/PMOS transistors are identical. In DC analysis, use the following equation:

$$I_D = \frac{1}{2} k'_{p,n} \frac{W}{L} (V_{GS} - V_{T0,p,n})^2.$$


Transistor parameters: $k_p' = \mu_p c_{ox} = 50 \mu A/V^2$, $k_n' = \mu_n c_{ox} = 100 \mu A/V^2$, $V_{An} = V_{Ap} = 100V$, $V_{T0,p} = -1V$, $V_{T0,n} = 1V$, $W_p = 16 \mu$, $L_p = 1 \mu$, $W_n = 8 \mu$, $L_n = 1 \mu$.

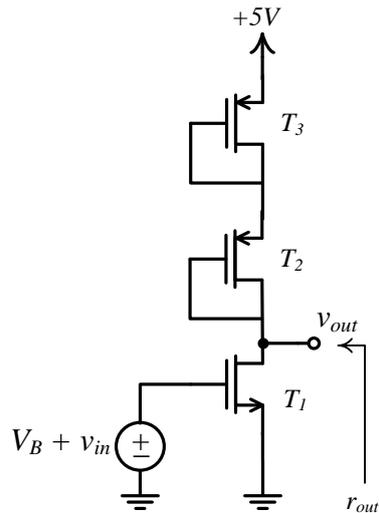- a. Determine the small signal gain v_{out}/v_{in} and the small signal output resistance r_{out} of the amplifier shown below.



Common Source Amplifier

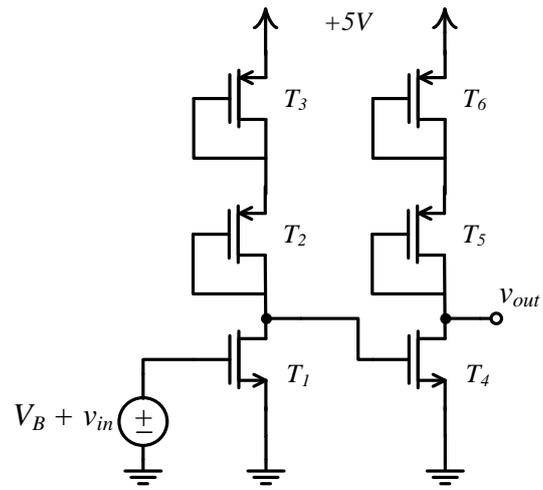- b. Determine the small signal gain v_{out}/v_{in} of the cascaded amplifier shown below.



Two-stage (Cascaded) Amplifier