




ITÜ
ELEKTRİK - ELEKTRONİK FAKÜLTESİ

Tarih : _____
Bölüm : _____
Ders : _____
No : _____
Adı Soyadı : _____
İmzası : _____


Soru	1	2	3	4	5	6	7	8	Toplam
Not									

HW-3

(1)

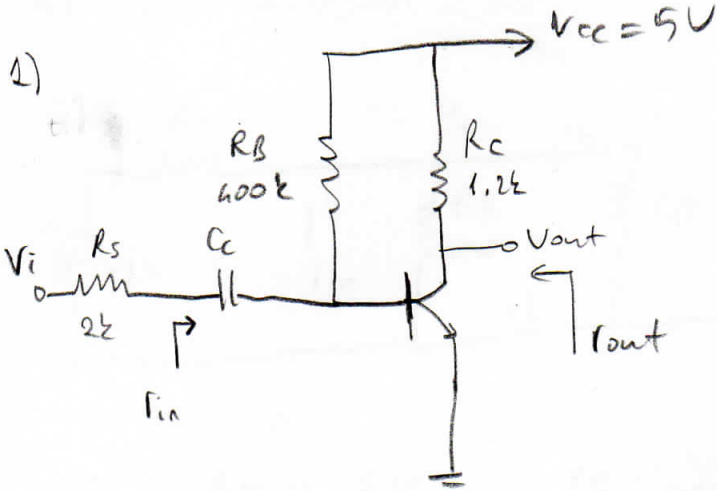

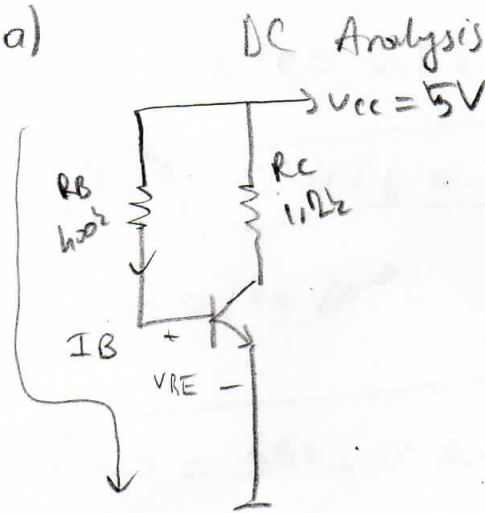$\beta = 200$
 $V_{BE} = 0,7$
 $V_T = 0,025V$
 $V_A = 100V$



loop equation in the direction of arrow;

$$V_{cc} - I_B \cdot R_B - V_{BE} = 0$$

$$5 - I_B \cdot 400k - 0,7V = 0 \Rightarrow I_B = \frac{4,3V}{400k} = 0,011mA$$

$$\boxed{V_B = 0,7} \Rightarrow V_B - V_E = V_{BE}$$

$$I_C = \beta \cdot I_B = 200 \cdot 0,011mA = 2,2mA$$

$$V_C = V_{cc} - R_C \cdot I_C = 5 - 1,2k \cdot 2,2mA = 2,36V$$

$$\boxed{V_C = 2,36V}$$

(10)




İTÜ
ELEKTRİK - ELEKTRONİK FAKÜLTESİ

Tarih : / /
Bölüm :
Ders :
No :
Adı Soyadı :
İmzası :

Soru	1	2	3	4	5	6	7	8	Toplam
Not									

b) AC analysis

(2)

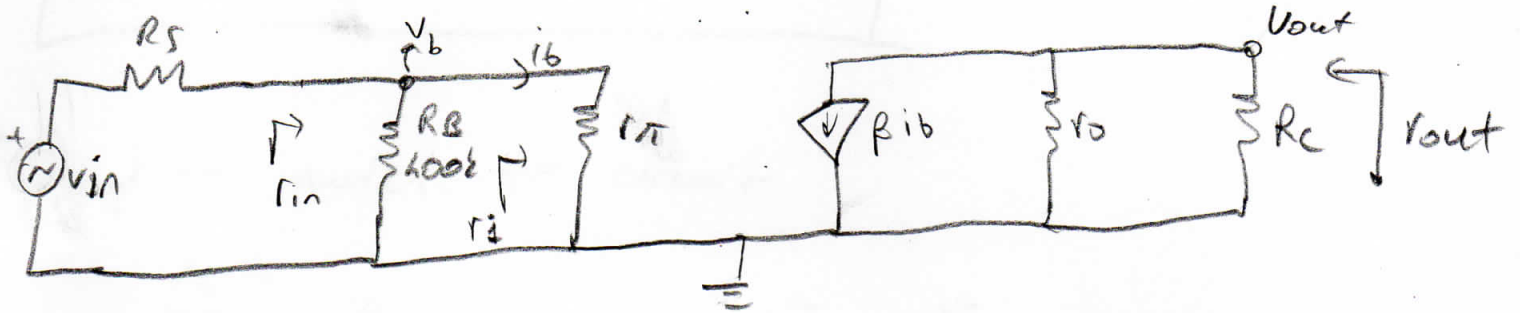

$$r_i = r_\pi = \beta r_e, \quad r_e = \frac{V_T}{I_C} = \frac{25 \text{ mV}}{2.2 \text{ mA}} = 11.4 \Omega$$

$$r_i = \beta \cdot r_e = 2.3 \text{ k}\Omega$$

$$r_{in} = r_i \parallel R_B \approx 2.2 \text{ k}\Omega$$

$$r_{out} = r_o \parallel R_C \Rightarrow r_o = \frac{V_A}{I_C} = \frac{100 \text{ V}}{2.2 \text{ mA}} \approx 45 \text{ k}\Omega$$

$$r_{out} = 45 \text{ k}\Omega \parallel 4.2 \text{ k}\Omega = 3.17 \text{ k}\Omega$$

$$\frac{V_{out}}{V_{in}} = \frac{V_b}{V_{in}} \cdot \frac{V_{out}}{V_b}$$

$$\frac{V_{out}}{V_b} = -g_m (R_C \parallel r_o) \rightarrow g_m = \frac{1}{r_e} \Rightarrow A_o = \frac{V_{out}}{V_b} = - \frac{3.17 \text{ k}\Omega}{11.4 \Omega} = -102.6$$

$$\frac{V_b}{V_{in}} = \frac{r_{in}}{r_{in} + R_S} = \frac{2.2 \text{ k}\Omega}{2.2 \text{ k}\Omega + 2 \text{ k}\Omega} = 0.52$$



İTÜ
ELEKTRİK - ELEKTRONİK FAKÜLTESİ


Tarih : / /
Bölüm :
Ders :
No :
Adı Soyadı :
İmzası :

Soru	1	2	3	4	5	6	7	8	Toplam
Not									

(3)

$$\frac{V_{out}}{V_{in}} = -102,6 \times 0,52 = -53,7$$

c) linear model for circuit

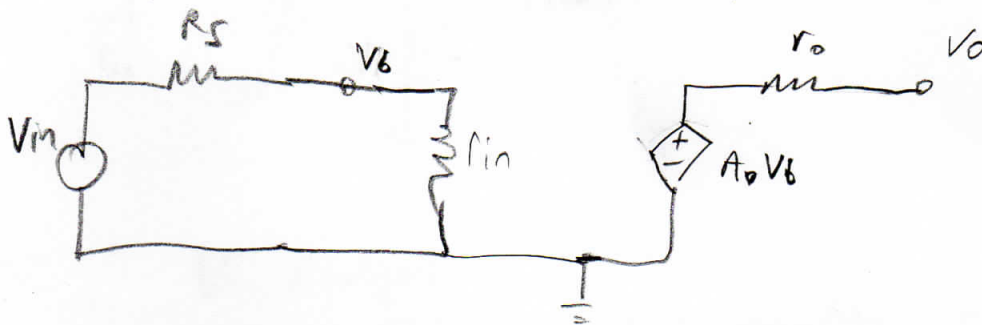

(5)

A_0 is the gain of transistor ($\frac{V_{out}}{V_b}$ in (b))


$$A_0 = -102,6$$

$$r_{in} = 2,2k\Omega$$

$$r_o = 1,17k\Omega$$

$$R_S = 2k\Omega$$

d) According to linear model

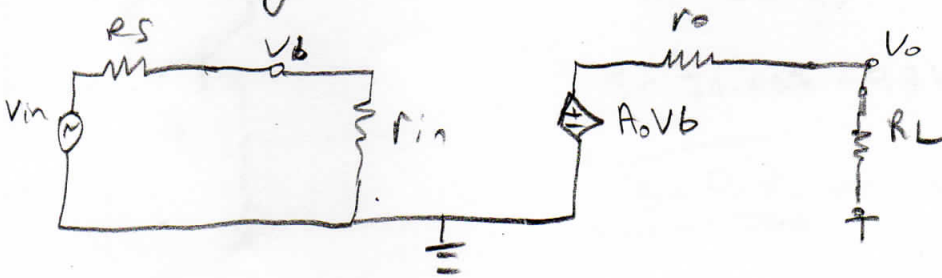

(5)

$$\frac{V_o}{V_{in}} = \frac{V_b}{V_{in}} \times \frac{V_o}{V_b} = \frac{r_{in}}{r_{in} + R_S} \times \frac{A_0 \cdot R_L}{R_L + r_o} = G_{RL}$$

Gain without R_L , $G_0 = \frac{V_o}{V_{in}} = \frac{r_{in}}{r_{in} + R_S} \times A_0$ (assuming open circuit)

$$G_{RL} \geq 0,9 G_0 \Rightarrow \frac{R_L}{R_L + r_o} \geq 0,9 \Rightarrow R_L \geq 0,9 (R_L + r_o)$$

$$0,1 R_L \geq 0,9 r_o$$

$$R_L \geq 9 r_o$$