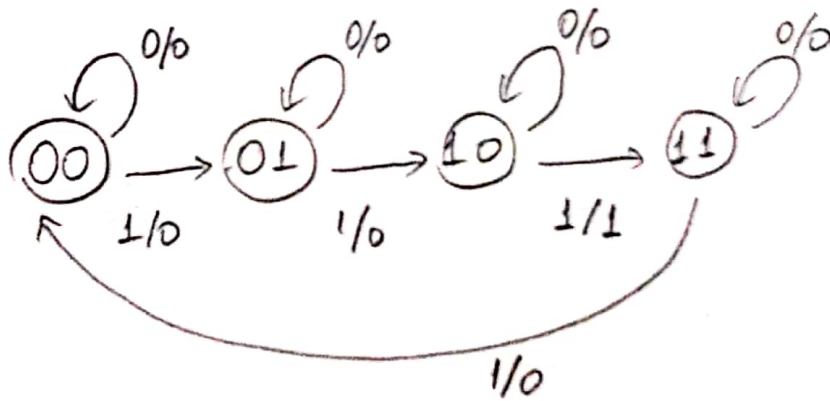


1-

a)

Cnt	Q_1	Q_0	Q_1^+	Q_0^+	y
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	1	0	0
0	1	1	1	1	0
1	0	0	0	1	0
1	0	1	1	0	0
1	1	0	1	1	0
1	1	1	0	0	1



b) Mealy-type

1

c)

Cnt	Q ₁	Q ₀	Q ₁ ⁺	Q ₀ ⁺	S ₁	R ₁	S ₀	R ₀
0	0	0	0	0	0	X	0	X
0	0	1	0	1	0	X	X	0
0	1	0	1	0	X	0	0	X
0	1	1	1	1	X	0	X	0
1	0	0	0	1	0	X	1	0
1	0	1	1	0	1	0	0	1
1	1	0	1	1	X	0	1	0
1	1	1	0	0	0	1	0	1

S₁

Q ₁ Q ₀	00	01	11	10
CNT				
0	0	0	X	X
1	0	1	0	X

$$S_1 = \text{CNT} \cdot \overline{Q_1} \cdot Q_0$$

R₁

Q ₁ Q ₀	00	01	11	10
CNT				
0	X	X	0	0
1	X	0	1	0

$$R_1 = \text{CNT} \cdot Q_1 \cdot Q_0$$

S₀

Q ₁ Q ₀	00	01	11	10
CNT				
0	0	X	X	0
1	1	0	0	1


$$S_0 = \text{CNT} \cdot \overline{Q_0}$$

R₀

Q ₁ Q ₀	00	01	11	10
CNT				
0	X	0	0	X
1	0	1	1	0

$$R_0 = \text{CNT} \cdot Q_0$$

(2)

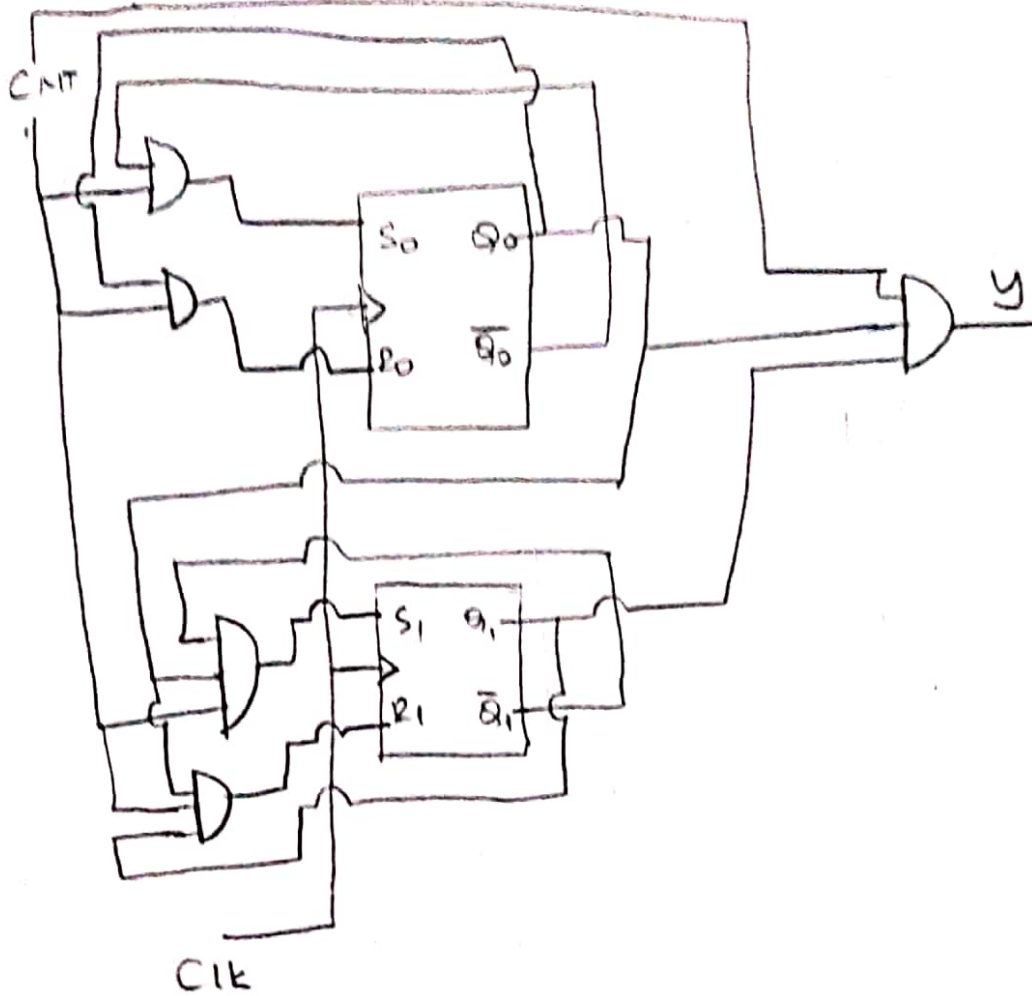

(2)

Q_3	Q_2	Q_1	Q_0	Q_3^+	Q_2^+	Q_1^+	Q_0^+	T_3	T_2	T_1	T_0
0	0	0	0	0	0	0	1	0	0	0	1
0	0	0	1	0	0	1	0	0	0	1	1
0	0	1	0	0	0	1	1	0	0	0	1
0	0	1	1	0	1	0	0	0	1	1	1
0	1	0	0	0	1	0	1	0	0	0	1
0	1	0	1	0	1	1	0	0	0	1	1
0	1	1	0	0	1	1	1	0	0	0	1
0	1	1	1	1	0	0	0	1	1	1	1
1	0	0	0	1	0	0	1	0	0	0	1
1	0	0	1	1	0	1	0	0	0	1	1
1	0	1	0	1	1	0	0	0	1	1	1
1	0	1	1	1	1	0	1	0	0	0	1
1	1	0	0	1	1	1	0	0	0	1	1
1	1	0	1	1	1	1	0	0	0	1	1
1	1	1	0	1	1	1	1	0	0	0	1
1	1	1	1	0	0	0	0	1	1	1	1

→ the circuit counts from 0 to 15. After 15, it starts 0 again.

(3)

T₃

Q ₁ Q ₀ \ Q ₂ Q ₁	00	01	11	10
00	0	0	0	0
01	0	0	1	0
11	0	0	1	0
10	0	0	0	0

T₃ = Q₂Q₁Q₀

T₂

Q ₁ Q ₀ \ Q ₃ Q ₂	00	01	11	10
00	0	0	1	0
01	0	0	1	0
11	0	0	1	0
10	0	0	1	0


T₂ = Q₁Q₀

T₁

Q ₁ Q ₀ \ Q ₂ Q ₁	00	01	11	10
00	0	1	1	0
01	0	1	1	0
11	0	1	1	0
10	0	1	1	0


T₁ = Q₀

T₀ = 1

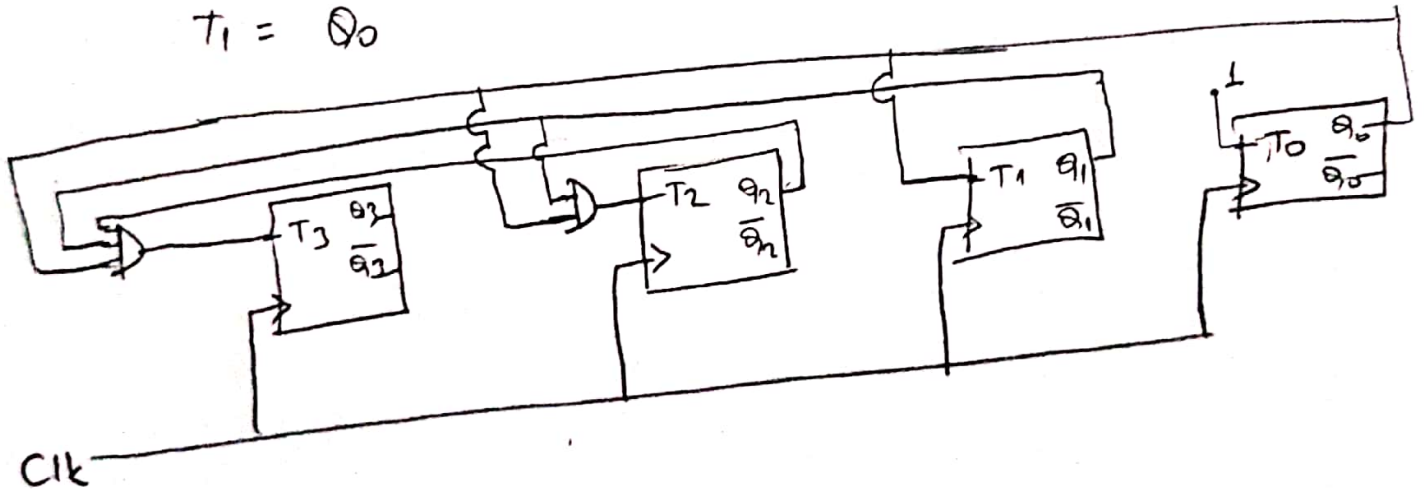

3-

a)

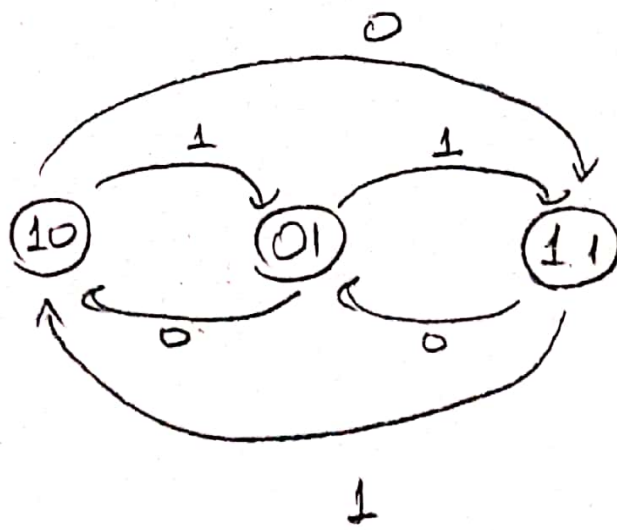

X	Q ₁	Q ₀	Q ₁ ⁺	Q ₀ ⁺	D ₁	D ₀
0	0	0	X	X	X	X
0	0	1	1	0	1	0
0	1	0	1	1	1	1
0	1	1	0	1	0	1
1	0	0	X	X	X	X
1	0	1	1	1	1	1
1	1	0	0	1	0	1
1	1	1	1	0	1	0

b)

D₁

Q ₁ , Q ₀	X=0	X=1
00	X	X
01	1	1
11	0	1
10	1	0

$$D_1 = \overline{Q_1} + X Q_0 + \overline{X} \overline{Q_0}$$

$$D_1 = \overline{Q_1} + X \odot Q_0$$


5

Do

		x	
		0	1
Q ₁ , Q ₀	00	0	1
	01	0	1
	11	1	0
	10	1	1

$$D_0 = \overline{Q_0} + Q_1 \overline{x} + x \overline{Q_1}$$

$$D_0 = \overline{Q_0} + Q_1 \oplus x$$

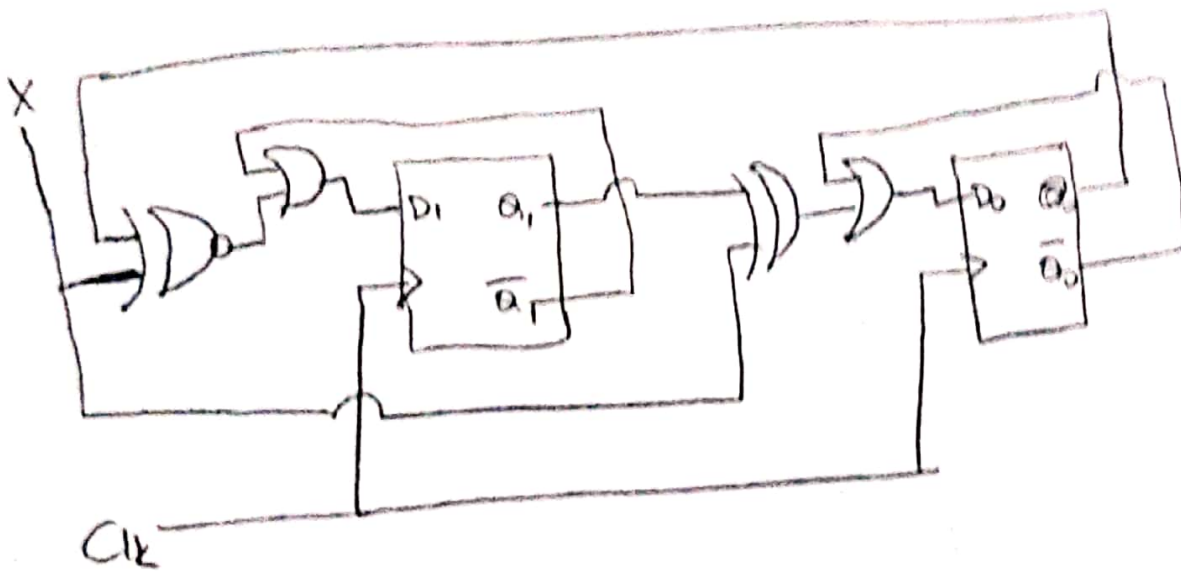

(6)