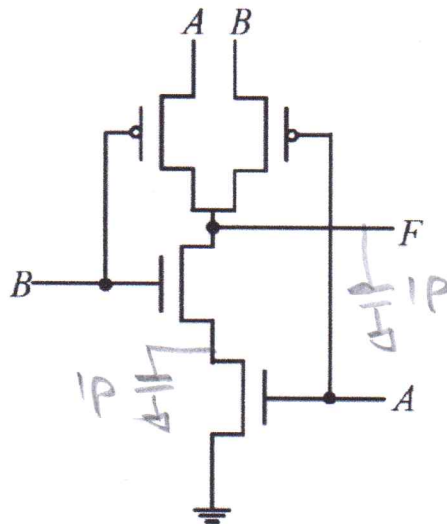


- Suppose that all NMOS transistors are identical and all PMOS transistors are identical.
Equivalent resistor for an NMOS transistor: $R_N = 8k\Omega$
Equivalent resistor for a PMOS transistor: $R_P = 24k\Omega$
 - Suppose that each circuit node (including outputs) has a capacitance value of $1pF$.
- a) Derive a Boolean expression for the output F in terms of the inputs A and B .
b) Calculate the worst-case and the best-case propagation delays, t_{PLH} and t_{PHL} values (total of 4 values).



40 a.)

A	B	F
0	0	0
0	1	1
1	0	1
1	1	0

$$F = A\bar{B} + \bar{A}B$$

40

b.)

60

$$t_{PLH-wc} = t_{PLH-sc} = 0,69 (1pF \parallel 24k\Omega) = 16,56ns$$

$$t_{PHL-wc} = 0,69 (16pF + 8k\Omega \parallel 1pF) = 16,56ns$$

$$t_{PHL-sc} = 0,69 ((24k\Omega \parallel 24k\Omega) \parallel 1pF) = 8,28ns$$