

EHB322E Digital Electronic Circuits Homework 2

Grading: 1) 30%, 2) 30%, 3) 40%

Deadline: 20/04/2020 (before 16:30)


Email your homeworks to the teaching assistant or submit via Ninova

- 1) Consider a buffer shown below. Use the following equations for your calculations.

Saturation region current-voltage equation: $I_D = \frac{1}{2} k'_{p,n} \frac{W}{L} (V_{GS} - V_{T0_{p,n}})^2$

Linear region current-voltage equation: $I_D = \frac{1}{2} k'_{p,n} \frac{W}{L} [2(V_{GS} - V_{T0_{p,n}})V_{DS} - V_{DS}^2]$

 Transistor parameters: $k_p' = \mu_p c_{ox} = 35 \mu\text{A}/\text{V}^2$, $k_n' = \mu_n c_{ox} = 98 \mu\text{A}/\text{V}^2$, $V_{TN} = 1\text{V}$, $V_{TP} = -0.5\text{V}$, $W_{N-1} = 5\mu$, $W_{N-2} = 5\mu$, $L_P = L_N = 1\mu$.



Buffer


- a) Find the maximum value of W_{P-1} satisfying that $V_{in} = 5\text{V}$ results in $V_{out} = 5\text{V}$.
 - b) Find the value of W_{P-2} if $V_{in} = 0\text{V}$ results in $V_{out} = 1\text{V}$.
 - c) Find the buffer's static power consumption values when $V_{in} = 0\text{V}$ and $V_{in} = 5\text{V}$.
- 2) Consider a buffer circuit consisting of two CMOS NAND gates, shown below. An external capacitor of 48fF is connected to the output. A signal switching from high to low is applied to the input.

Equivalent resistor for an NMOS transistor: $R_N = (12\text{k}\Omega) / (W/L)_N$

Equivalent resistor for a PMOS transistor: $R_P = (24\text{k}\Omega) / (W/L)_P$

Gate capacitors $C_{GS-N} = c_{ox} W_N L_N$ and $C_{GS-P} = c_{ox} W_P L_P$; neglect C_{GD} capacitors.

 Transistor parameters: $c_{ox} = 1\text{ fF}/\mu\text{m}^2$, $L_N = L_P = 1\mu$, $W_{N1} = 2\mu$, $W_{P1} = 3\mu$, $W_{N2} = 4\mu$, $W_{P2} = 6\mu$.



Digital circuit with two CMOS NAND gates

- a) Implement a NAND gate with a Boolean function $f = \overline{x_1 x_2}$ using CMOS transistors. If inputs of a NAND gate are shorted, as we use in our circuit, then find its Boolean function. Draw the CMOS implementation of the above circuit.
- b) Find the **total propagation delay value** between the input and the output.
- You should consider C_{GS} capacitors as well as the external $C=48fF$ capacitor
 - Do not consider capacitors at nodes other than the node of gate inputs/outputs.
- 3) For a specific technology and a specific supply voltage, a CMOS inverter with parameters $W_P=1u$, $W_N=1u$, $L_P=1u$, $L_N=1u$, and a total output load capacitor of $1 fF$ has $t_{PHL}=1ns$ and $t_{PLH}=2ns$. By considering the same technology and the supply voltage,
- a) Implement $f = x_1 x_2 \overline{x_3} + x_1 \overline{x_2} x_3 + \overline{x_1} x_2 x_3 + \overline{x_1} x_4$ with a **CMOS circuit** using **minimum** number of transistors. Draw the circuit. How many PMOS and NMOS transistors do you use?
- b) Select $W_P=4u$ for all PMOS transistors and $W_N=2u$ for all NMOS transistors of your CMOS circuit. Find the **worst case (largest) and the best case (smallest) t_{PHL} and t_{PLH}** values if a total output load capacitor is $2 fF$. Neglect internal node capacitors. You should report 4 delay values.