

Student Name:

Instructor: Mustafa Altun

Student ID:

Date: 7/10/2019

EHB 205E: Introduction to Logic Design

Quiz 1

Duration: 30 Minutes

Grading: 1) 20%, 2) 40%, 3) 40%,



Quiz is in closed-notes and closed-books format

For your answers please use the space provided in the exam sheet

GOOD LUCK!

1. Answer the following statements with T(true) or F(false) only.
(do not guess: points are deducted for wrong answers. If you do not know the answer, leave it blank)
- a) ____ Finite decimal fraction can be always converted to finite binary fraction
 - b) ____ Finite hexadecimal fraction can be always converted to finite binary fraction
 - c) ____ (The population of Burundi was below 1 million in 2013) NAND (banana is tastier than apple)
 - d) ____ A circuit performing a binary addition of two n -bit numbers needs n outputs.
 - e) ____ A circuit performing a binary multiplication of two n -bit numbers needs $2n$ outputs.

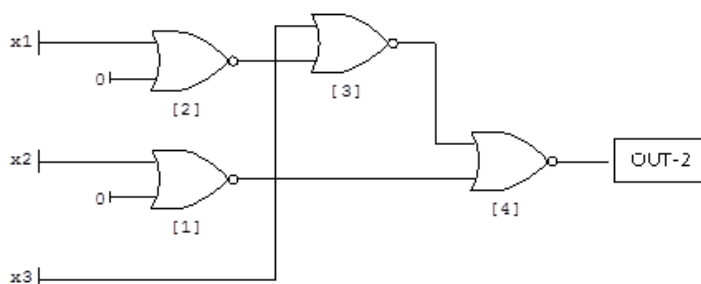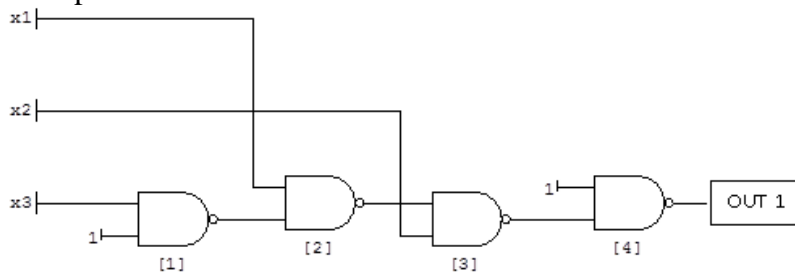2. Consider the below two circuits having three inputs x_1 , x_2 , and x_3 as well as 0 and 1 inputs. The one consisting of NAND2 gates has an output OUT 1 and the other one having NOR2 gates has an output OUT 2.



- a) Derive Boolean expressions of OUT 1 and OUT 2 in terms x_1 , x_2 , and x_3 , and their negations.

b) Find XOR of OUT 1 and OUT 2

3. Obtain a minimal sum-of-products (SOP) expression for f using a **Karnaugh** map.

$$f = \overline{x_1 \overline{x_2} \overline{x_3}} + \overline{x_1 \overline{x_2} \overline{x_4}} + \overline{\overline{x_1} x_2 x_3 \overline{x_4}} + \overline{\overline{x_1} x_2 \overline{x_3} x_4}$$