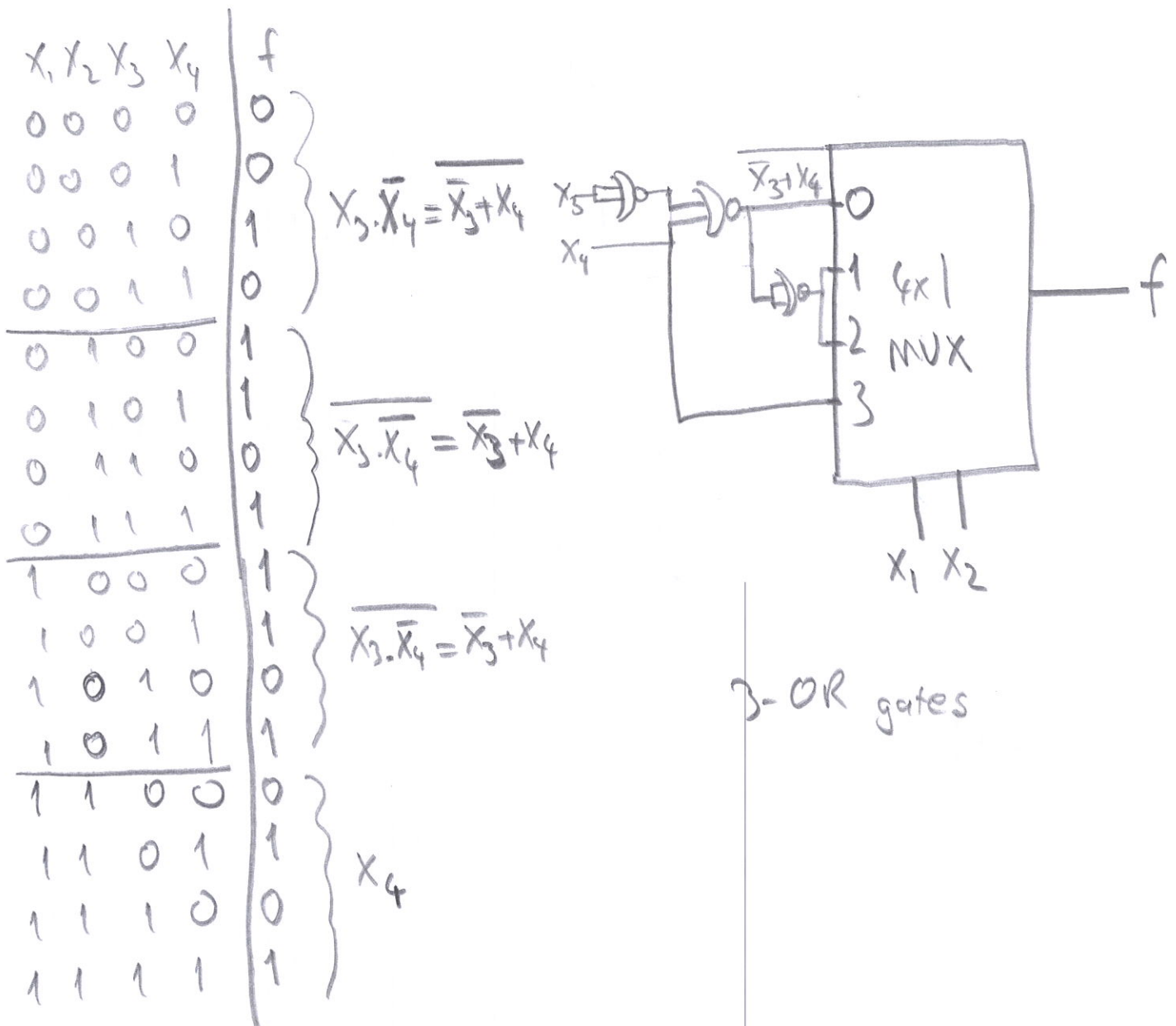



# Solutions

1. Implement a 4-variable Boolean function  $f(x_1, x_2, x_3, x_4) = \sum(2, 4, 5, 7, 8, 9, 11, 13, 15)$  using a **single 4-to-1 multiplexer** and minimal number of **two-input NOR gates**. Use  $x_1$  and  $x_2$  as select input lines in the multiplexer. Use only variables  $x_1, x_2, x_3, x_4$  as inputs (**not their negated forms**).




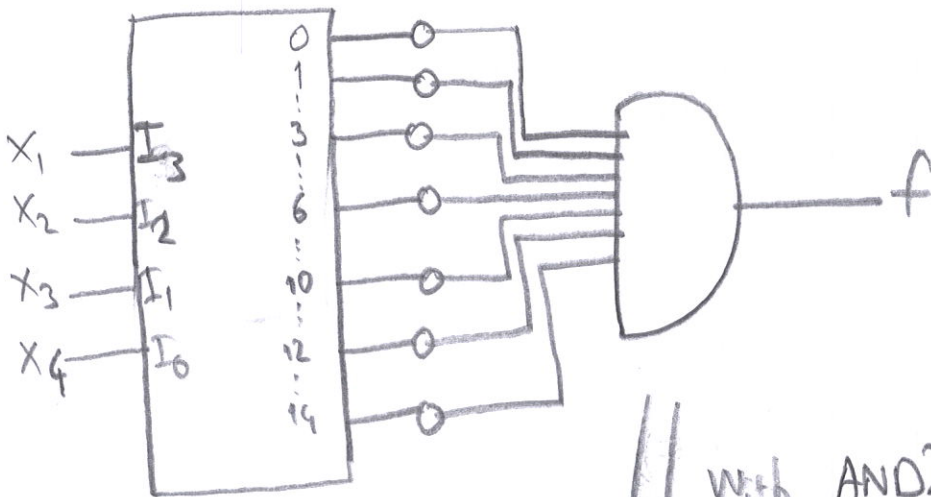2. Implement a 4-variable Boolean function  $f(x_1, x_2, x_3, x_4) = \sum (2,4,5,7,8,9,11,13,15)$  using a **single decoder** and minimal number of **two-input NAND gates**. Use only variables  $x_1, x_2, x_3, x_4$  as inputs (**not their negated forms**).

$$\Sigma = (2,4,5,7,8,9,11,13,15) = \Pi (0,1,3,6,10,12,14)$$



with AND-2 gates

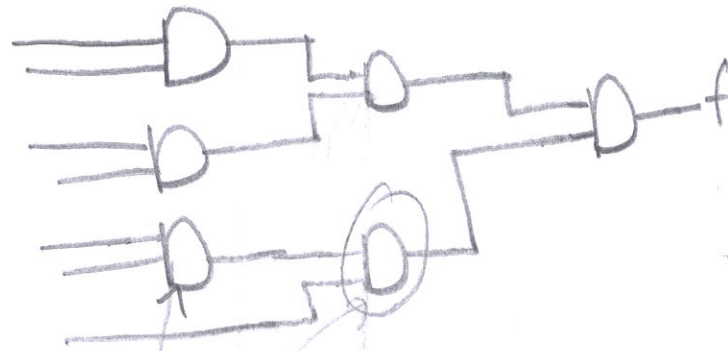

(6 AND gates)



1 AND-2 gate  $\equiv$  2 NAND-2 gates

6 AND-2 gates  $\equiv$  12 NAND-2 gates

$$12 \text{ NAND-2 gates (for AND-7)} + 7 \text{ NAND-2 gates (for inverters)} = \boxed{19 \text{ gates}}$$