


Student Name:

Student ID:

# EHB262E Electronics II

## Homework 4

Deadline: before the final exam

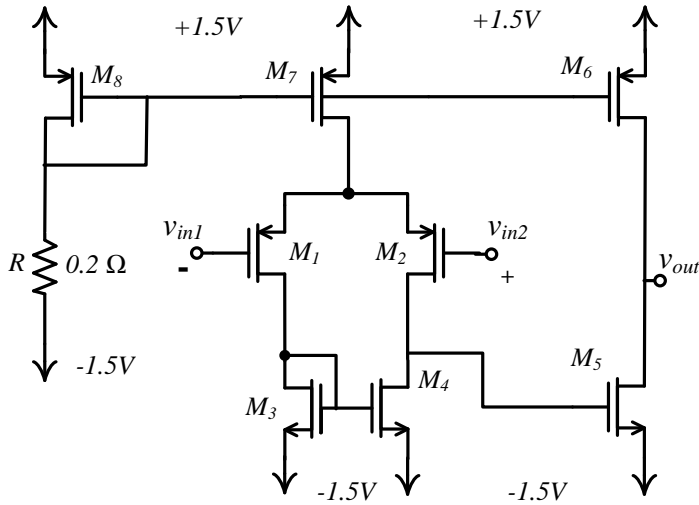


Transistor	L (μm)	W (μm)
M <sub>1</sub>	1	50
M <sub>2</sub>	1	50
M <sub>3</sub>	1	20
M <sub>4</sub>	1	20
M <sub>5</sub>	1	20
M <sub>6</sub>	1	10
M <sub>7</sub>	1	20
M <sub>8</sub>	1	20

Operational Amplifier

Consider an operational amplifier (OP-AMP) shown above. Assume that all MOSFETs are operating in saturation region. Also assume that input and output DC operating points are all **zero**. Transistors have the following parameters:  $k_p' = \mu_p c_{ox} = 45 \text{ A/V}^2$ ,  $k_n' = \mu_n c_{ox} = 80 \text{ A/V}^2$ ,  $V_{An} = 500$ ,  $V_{Ap} = 50 \text{ V}$ ,  $V_{T0,p} = -0.9 \text{ V}$ ,  $V_{T0,n} = 1 \text{ V}$ .

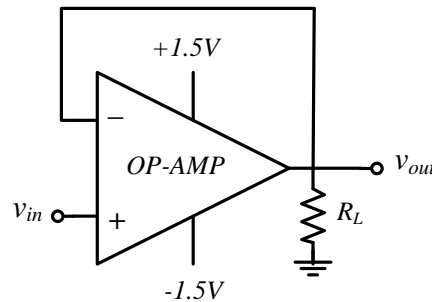- a) Calculate the small signal differential gain  $v_{out} / (v_{in2} - v_{in1})$  of the amplifier for the following cases. (You can assume that currents flowing on  $M_7$  and  $M_6$  are 10A and 5A, respectively).
  - **Case 1:** The amplifier drives a load resistance of 1Ω ( $R_L = 1\Omega$ ).
  - **Case 2:** The amplifier drives a load resistance of 1kΩ ( $R_L = 1\text{k}\Omega$ ).
- b) Use the OP-AMP as a voltage follower, shown below. Construct this circuit in SPICE. Apply a sine signal to the input ( $v_{in}$ ) with 1mV peak-to-peak amplitude and 1kHz frequency. Print out  $v_{out}$  and  $v_{in}$  in time domain for different load resistance values:  $R_L = 1\Omega$  and  $R_L = 1\text{k}\Omega$ . Does  $v_{out}$  follow  $v_{in}$  for both cases? Why? Justify your answer using the results calculated in a).
  - Use FDR840P and FDR6580 SPICE models for PMOS and NMOS transistors, respectively.



Voltage follower

Grading: a) 50%, b) 50%,

Note: Do not forget to attach SPICE **output file** prints to your homework!