

Student Name:

Instructor: Mustafa Altun

Student ID:

Date: 24/12/2021

EHB205E Introduction to Logic Design

MIDTERM II

Duration: 120 Minutes

Grading: 1) 20%, 2) 20%, 3) 25%, 4) 35%

Exam is in closed-notes and closed-books format; calculators are allowed

For your answers please use the space provided in the exam sheet

GOOD LUCK!

- 1) Consider Boolean functions $f_1(x_1, x_2, x_3) = \sum (0,1,3,5,6,7)$ and $f_2(x_4, x_5, x_6) = \sum (2,3,4,5,6,7)$. Implement $f = f_1 + f_2$ using **two 3-to-8 decoders** and minimal number of **two-input NOR gates**.

2) Consider a **6-to-1 multiplexer** having inputs $I_0, I_1, I_2, I_3, I_4, I_5$; select input S_0, S_1, S_2 ; and the output OUT.

If $(S_0, S_1, S_2) = (0, 0, 0)$ then $OUT = I_0$;

If $(S_0, S_1, S_2) = (0, 0, 1)$ then $OUT = I_1$;

If $(S_0, S_1, S_2) = (0, 1, 0)$ then $OUT = I_2$;


If $(S_0, S_1, S_2) = (0, 1, 1)$ then $OUT = I_3$;

If $(S_0, S_1, S_2) = (1, 0, 0)$ then $OUT = I_4$;

If $(S_0, S_1, S_2) = (1, 0, 1)$ then $OUT = I_5$.

Implement this 6-to-1 multiplexer multiplier using **minimal number of 2-to-1 multiplexers**.

 3) Consider a sequential circuit shown below.



- a) For which input values of M, N, and G, **outputs P and Q hold their previous values?**
- b) Obtain a minimal sum-of-products (SOP) expressions for **P and Q** in terms of M, N, and G as well as the previous values of P and Q.

- 4) Consider a flip-flop consisting of four NAND gates, shown below. Suppose that each of the NAND gates has a delay of **2ns**. Suppose that initial values of Q and Q' are 0 and 1, respectively. Sketch the **waveforms at the outputs Q and Q'** if the input signals A and CLK shown below are applied.

