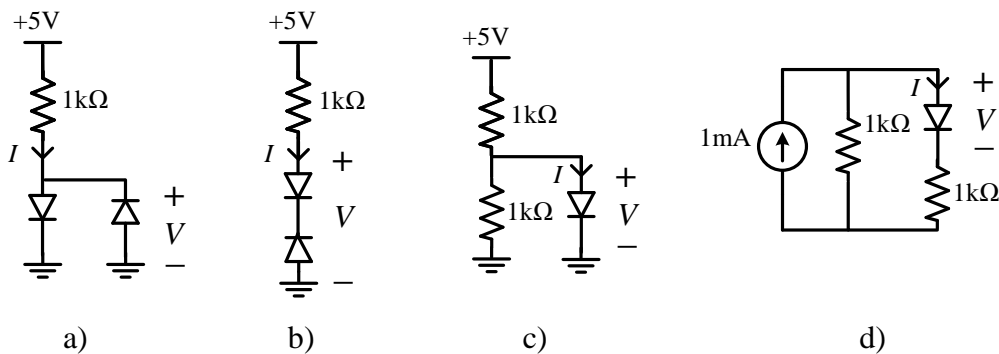


EHB222E Introduction to Electronics

Homework 1

Deadline: 02/03/2015 (before the lecture)

1. Silicon is doped with Boron having a concentration of $10^{11} / \text{cm}^3$. Calculate the free electron and hole concentrations, n and p , respectively. Suppose that $n_i = 4 \cdot 10^{10} / \text{cm}^3$.
2. Assume that you a p-n diode has the following specific resistances: $\rho_n = 0,35 \Omega\text{cm}$ and $\rho_p = 0,7 \Omega\text{cm}$. Additionally, $n_i = 10^{10} / \text{cm}^3$, $q = 1,6 \cdot 10^{-19} \text{C}$, $\epsilon_{r\text{-Si}} = 12$, $\epsilon_o = 8,85 \cdot 10^{-12} \text{F/m}$ ($\epsilon_{\text{Si}} = \epsilon_{r\text{-Si}} \epsilon_o$), $V_T = 25 \text{mV}$. Also $D_n = 36 \text{cm}^2/\text{s}$, $D_p = 16 \text{cm}^2/\text{s}$, $\tau_n = \tau_p = 0,8 \mu\text{sec}$.
 - a. Find the built in voltage V_o .
 - b. Find the depletion region width in zero bias (no voltage applied).
 - c. For a junction area of $0,1 \text{mm}^2$, calculate the current through your diode when it is forward biased at $0,7 \text{V}$.
3. A p-n diode is modeled with the exponential model. The diode currents are measured $1,36 \text{mA}$ and $7,20 \text{mA}$ when $0,7 \text{V}$ and $0,75 \text{V}$ applied, respectively. Determine the saturation current I_s and the ideality factor n (from nV_T). Suppose that $V_T = 25 \text{mV}$.
4. Find the values of I and V for the circuits shown. Use the **ideal I-V model** for diodes.



5. Find the current and voltage values of the Zener diodes I_{D1} , V_{D1} , I_{D2} , and V_{D2} . Use the constant drop model, shown in Figure 2, for Zener diodes.

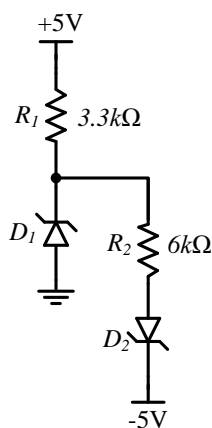


Figure 1

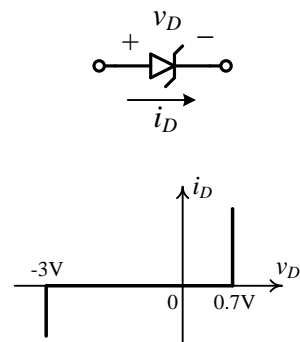


Figure 2: 0,7 V forward bias and 3 V Zener voltages

6. Use a constant drop model for the Zener diode in Figure 1. The model has 0,7 V forward bias and 2 V Zener ($V_Z=2V$) voltage. An input signal, shown in Figure 2, is applied. Sketch v_o , i_{D1} , and i_{D2} , in time domain. Justify your answer.

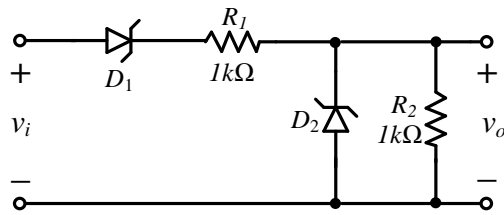


Figure 1

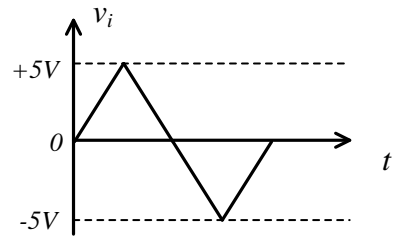


Figure 2

Grading: 1)10 %, 2)15 %, 3)15 %, 4)20 %, 5)20 %, 6)20 %