

Student Name:

Instructor: Mustafa Altun

Student ID:

Date: 16/03/2015

EHB222E Introduction to Electronics MIDTERM I

Duration: 120 Minutes

Grading: 1) 15%, 2) 30%, 3) 25%, 4) 30%

Exam is in closed-notes and closed-books format; calculators are allowed



For your answers please use the space provided in the exam sheet

GOOD LUCK!


1. The current-voltage equation of a p-n diode is given as $I_D = I_S(e^{V_D/nV_T} - 1)$ where $I_S = Aqn_i^2 \left(\frac{D_p}{L_p N_D} + \frac{D_n}{L_n N_A} \right)$. Additionally, $L_p = \sqrt{D_p \tau_p}$ and $L_n = \sqrt{D_n \tau_n}$. The diode conducts current of -10^{-15} A when -3V voltage applied. Determine the **junction area A**. with a unit of μm^2 .

Parameters: $n_i = 2,5 \cdot 10^{10} / \text{cm}^3$, $N_D = 10^{17} / \text{cm}^3$, $N_A = 10^{15} / \text{cm}^3$, $q = 1,6 \cdot 10^{-19}$ C, $1 \leq n \leq 2$,
 $V_T = 25$ mV, $D_n = 100 \text{ cm}^2/\text{s}$, $D_p = 16 \text{ cm}^2/\text{s}$, $\tau_n = \tau_p = 1 \text{ } \mu\text{sec}$.

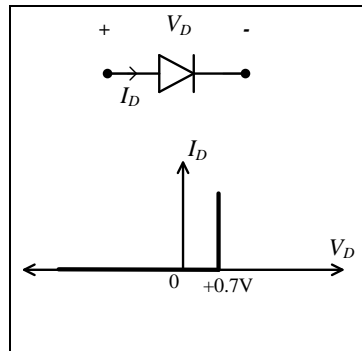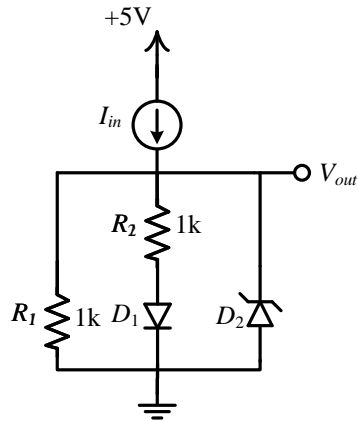2. For the diodes, use the models shown below; the regular diode model has **0,7V** forward bias voltage; the Zener diode model has **-3V** breakdown voltage.
- Determine the minimum positive value of I_{in} to make D_1 conduct current.
 - Determine the minimum positive value of I_{in} to make D_2 conduct current.
 - Sketch V_{out} versus I_{in} ($0 \leq I_{in} \leq 10\text{mA}$).





Regular Diode Model

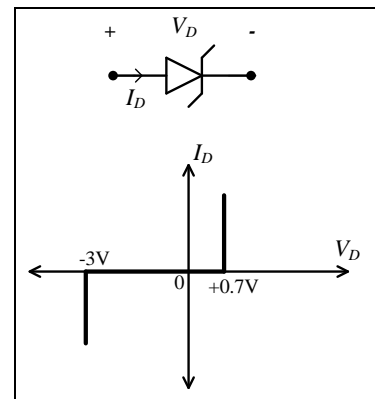

Zener Diode Model

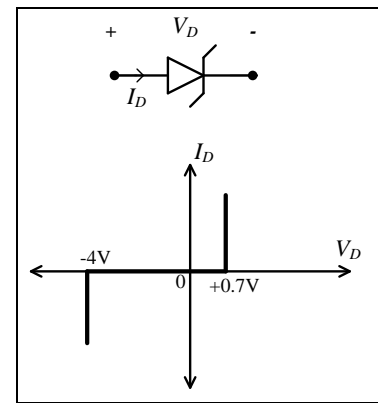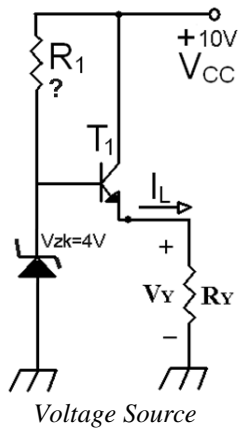3. Consider a voltage source shown below. It drives a load with a minimum value of 100Ω ; $R_Y \geq 100\Omega$. Its output voltage should be around $3.3V$; $V_Y \approx 3.3V$. Determine the maximum value of R_1 .



Zener Diode Model, $V_{zk}=4V$

Transistor parameters: $V_{BE} = 0.7$, $\beta = 100$, $V_A = \infty$.

4. For the circuit shown below, suppose that all of the transistors are in forward active region; $|V_{BE}| = 0.7\text{V}$, $\beta = 200$, and $|V_A| = \infty$ for all transistors.
- If $V_i = 0\text{V}$, determine the values of I_{C1} , I_{C2} , and I_{C3} .
 - If $V_i = 0\text{V}$ and $I_{C4} = 0.5\text{mA}$, determine the value of R_{E4} .

