

Student Name:

Instructor: Mustafa Altun

Student ID:

Date: 19/11/2021

EHB 205E: Introduction to Logic Design

MIDTERM I

Duration: 120 Minutes

Grading: 1) 15%, 2) 30%, 3) 25%, 4) 30%

Exam is in closed-notes and closed-books format; calculators are allowed

For your answers please use the space provided in the exam sheet


GOOD LUCK!

- 1) Consider a 4-variable Boolean function $f(x_1, x_2, x_3, x_4) = \sum(1,3,4,5,9,11,12,13,14,15)$; x_1 is the most significant bit. Obtain a minimal sum-of-products (SOP) expression for f using a **Karnaugh** map. Show all prime and essential prime implicants.

2) Consider a 6-variable Boolean function $f = f_1(x_1, x_2, x_3, x_4) \cdot f_2(x_4, x_5, x_6)$ where $f_1 = \prod (1, 2, 3, 5, 7, 12, 14)$ - x_1 is the most significant bit, and $f_2 = \prod (3, 4, 5, 6, 7)$ - x_4 is the most significant bit.

- a) Obtain a minimal product-of-sum (POS) expression for f .
- b) Implement f using only **two-input NAND** (NAND-2) gates; use minimal number of gates. Use only variables as inputs (**not their negated forms**).

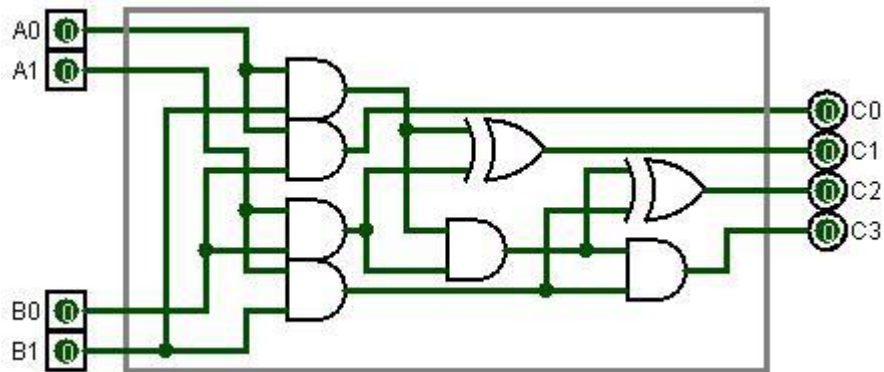- 3) Consider a circuit consisting of AND-2 and XOR-2 gates with 4 inputs , **A0, A1, B0, B1**, and 4 outputs, **C0, C1, C2, C3**.



- a) Derive truth table of this circuit.
 b) Suppose that for a certain application, always **A0=1** and **B0=0**. For this scenario, simplify the circuit by only using NOR-2 gates.

- 4) Consider 4 binary inputs representing decimal numbers from 0 to 15. Also consider a 7-segment display as shown below. It only shows two letters: H (stands for high), and L (stands for low). If the decimal number is below 5, the display shows L; if the decimal number above 10 the display shows H; otherwise (5, 6, 7, 8, 9, 10) what the segment shows, does not matter. Design a circuit consisting of minimal number of NAND-2 gates for this operation. Note that the circuit has 4 inputs and 7 outputs; 7 outputs of the circuit are connected to 7 segments **a**, **b**, **c**, **d**, **e**, **f**, and **g**. If a segment output is logic 1 then the corresponding segment is illuminated or lit.

