


# EHB205E Introduction to Logic Design

## Homework 4

Deadline: 21/01/2022 (submit using Ninova before 9:30)
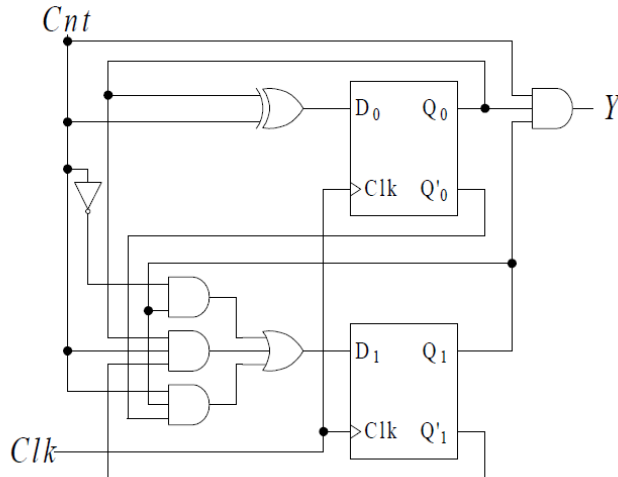
### 1. SEQUENTIAL CIRCUITS: CIRCUITS TO STATES


Consider a sequential circuit with an input  $Cnt$  and an output  $Y$ , shown below.



- a) Obtain **state diagrams** and **state tables** of the circuit.
- b) Determine whether this circuit is **Mealy** or **Moore** machine.
- c) Implement the diagram or table found in a), using positive edge triggered S-R flip-flops.
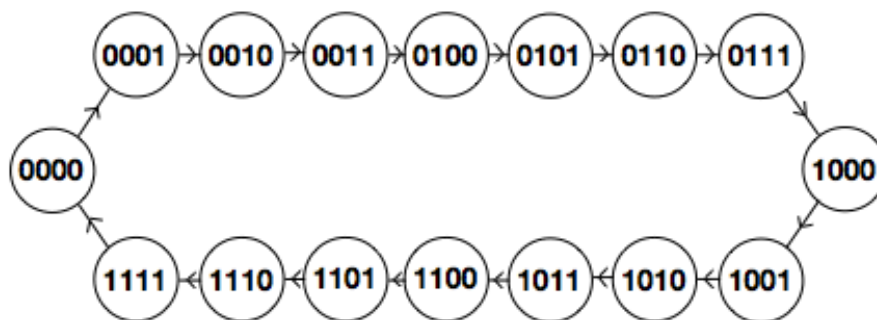
### 2. SEQUENTIAL CIRCUITS: STATES TO CIRCUITS

Consider a state diagram shown below. Implement this state diagram using T (toggle) flip-flops and AND gates. What is the purpose of the circuit?



### 3. STATE MACHINE SYNTHESIS

Design a counter with a control input. When the input is high, the counter should sequence through three states: 10, 01, 11 and repeat. When the input is low the counter should sequence through the same states in the opposite order 11, 01, 10 and repeat.

- a) Draw the state diagram and state transition table.
- b) Implement the counter using D flip-flops and gates.

Grading: 1) 40% 2)30% 3)30%

Note: Return through Ninova.