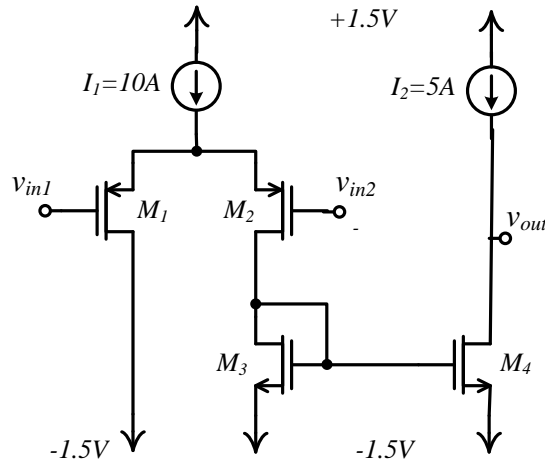


Student Name:

Student ID:

EHB262E Electronics II Homework 3


Deadline: 20/12/2012 (before the lecture)



Transistor	L (μm)	W (μm)
M_1	1	50
M_2	1	50
M_3	1	20
M_4	1	20

Differential Amplifier with Ideal Current Sources

Consider a differential amplifier shown above. Replace the ideal current sources with the transistor-level current sources shown below, so you have a differential amplifier with 7 transistors and a resistor. Answer all the following questions considering this amplifier. Assume that all MOSFETs are operating in saturation region. Also assume that input and output DC operating points are all **zero**. Transistors have the following parameters: $k_p' = \mu_p c_{ox} = 45\text{A/V}^2$, $k_n' = \mu_n c_{ox} = 80\text{A/V}^2$, $V_{An} = 500$, $V_{Ap} = 50\text{V}$, $V_{T0,p} = -0.9\text{V}$, $V_{T0,n} = 1\text{V}$.

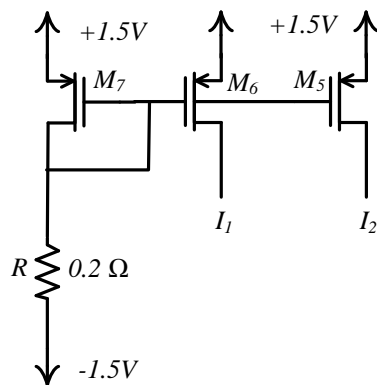

Transistor	L (μm)	W (μm)
M_5	1	10
M_6	1	20
M_7	1	20

Current Sources in Transistor-level

- a) Calculate the small signal differential gain $v_{out} / (v_{in1} - v_{in2})$.
 - Assume that $I_1 = 10\text{A}$ and $I_2 = 5\text{A}$.
- b) Calculate the small signal common-mode gain v_{out} / v_{in} where $v_{in1} = v_{in2} = v_{in}$.
 - Assume that $I_1 = 10\text{A}$ and $I_2 = 5\text{A}$.
- c) Calculate **CMRR**.

d) To verify your calculated result, find $v_{out} / (v_{in1} - v_{in2})$, v_{out} / v_{in} , and **CMRR** using SPICE.

- Use FDR840P and FDR6580 SPICE models for PMOS and NMOS transistors, respectively.
- To make the output DC operating point zero, apply a DC offset to v_{in1} (It should be around 7.8mV).
- Use a sine signal with 1mV peak-to-peak amplitude and 1kHz frequency as a small signal voltage source.

Grading: a) 20%, b) 20%, c) 10%, d) 50%

Note: *Do not forget to attach SPICE **output file** prints to your homework!*