

Student Name:

Instructor: Mustafa Altun

Student ID:

Date: 02/06/2022

## EHB322E Digital Electronic Circuits QUIZ II

*Duration: 60 Minutes*

*For your answers please use the space provided in the exam sheet*

*GOOD LUCK!*

Consider the circuit having the output  $F$  and the inputs  $A$  and  $B$  shown below.

- Suppose that all NMOS transistors are identical and all PMOS transistors are identical.  
*Equivalent resistor for an NMOS transistor:  $R_N = 8\text{k}\Omega$*   
*Equivalent resistor for a PMOS transistor:  $R_P = 24\text{k}\Omega$*
- Suppose that each circuit node (including outputs) has a capacitance value of  $1\text{pF}$ .

Calculate the worst-case and the best-case propagation delays at the output,  $t_{PLH}$  and  $t_{PHL}$  values (total of 4 values).

